

# Chapter 2

# Smith Chart and Impedance Matching



Trinh Xuan Dung, PhD  
[dung.trinh@hcmut.edu.vn](mailto:dung.trinh@hcmut.edu.vn)

Department of Telecommunications  
Faculty of Electrical and Electronics Engineering  
Ho Chi Minh city University of Technology

# Contents

- 1. Introduction**
- 2. Smith Chart**
- 3. Smith Chart Applications**
- 4. Y Smith Chart**
- 5. Impedance Matching**


## Problems

# 1. Introduction

- ❖ Many of calculations required to solve T.L. problems involve the use of complicated equations.
- ❖ Smith Chart, developed by Phillip H. Smith in 1939, is a graphical aid that can be very useful for solving T.L. problems.
- ❖ The Smith chart, however, is more than just a graphical technique as it provides a useful way of visualizing transmission line phenomenon without the need for detailed numerical calculations.
- ❖ A microwave engineer can develop a good intuition about transmission line and impedance-matching problems by learning to think in terms of the Smith chart.
- ❖ From a mathematical point of view, the Smith chart is simply a representation of all possible complex impedances with respect to coordinates defined by the reflection coefficient.
- ❖ The domain of definition of the reflection coefficient is a circle of radius 1 in the complex plane. This is also the domain of the Smith chart.
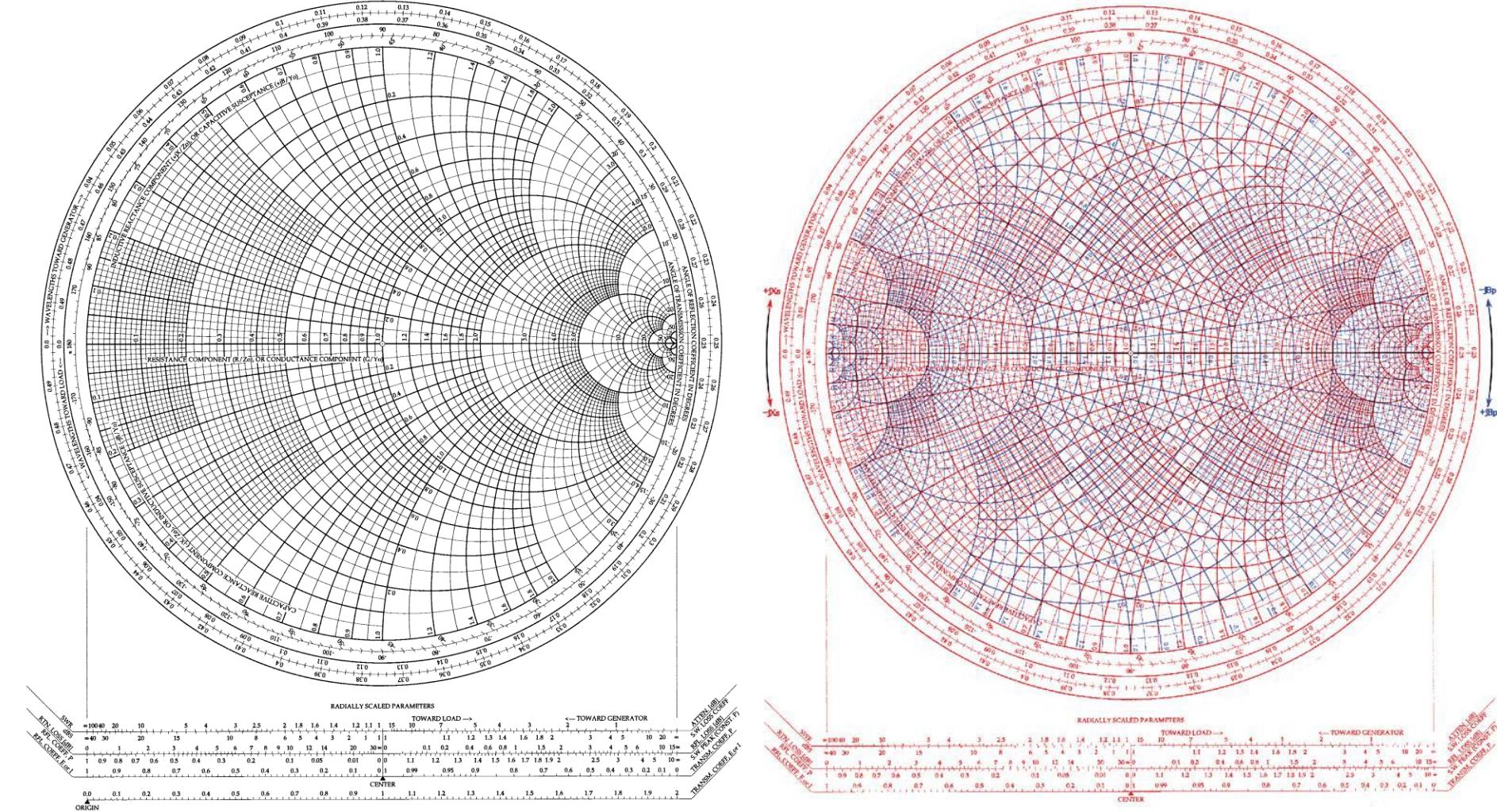
# 1. Introduction


**The Complete Smith Chart**  
Black Magic Design


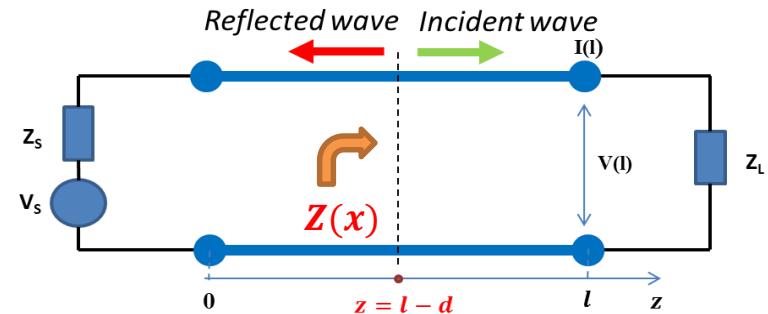
# 2. Smith Chart

- We start from the general definition of reflection coefficient:

$$\Gamma = \frac{Z - Z_0}{Z + Z_0} = \frac{Z/Z_0 - 1}{Z/Z_0 + 1} = \frac{z - 1}{z + 1}$$



- Now  $z$  can be written as:

$$z = \frac{1 + \Gamma}{1 - \Gamma} = \frac{1 + \operatorname{Re}(\Gamma) + j \operatorname{Im}(\Gamma)}{1 - \operatorname{Re}(\Gamma) - j \operatorname{Im}(\Gamma)} = \frac{1 - \operatorname{Re}^2(\Gamma) - \operatorname{Im}^2(\Gamma) + 2j \operatorname{Im}(\Gamma)}{[1 - \operatorname{Re}(\Gamma)]^2 + \operatorname{Im}^2(\Gamma)}$$

where:  $z = r + jx$  . Then:  $r = \frac{1 - \operatorname{Re}^2(\Gamma) - \operatorname{Im}^2(\Gamma)}{[1 - \operatorname{Re}(\Gamma)]^2 + \operatorname{Im}^2(\Gamma)}$        $x = \frac{2 \operatorname{Im}(\Gamma)}{[1 - \operatorname{Re}(\Gamma)]^2 + \operatorname{Im}^2(\Gamma)}$

- These equations can be re-arranged into:


$$\left( \operatorname{Re}(\Gamma) - \frac{r}{1+r} \right)^2 + \operatorname{Im}^2(\Gamma) = \left( \frac{1}{1+r} \right)^2$$

$$(\operatorname{Re}(\Gamma) - 1)^2 + \left( \operatorname{Im}(\Gamma) - \frac{1}{x} \right)^2 = \left( \frac{1}{x} \right)^2$$
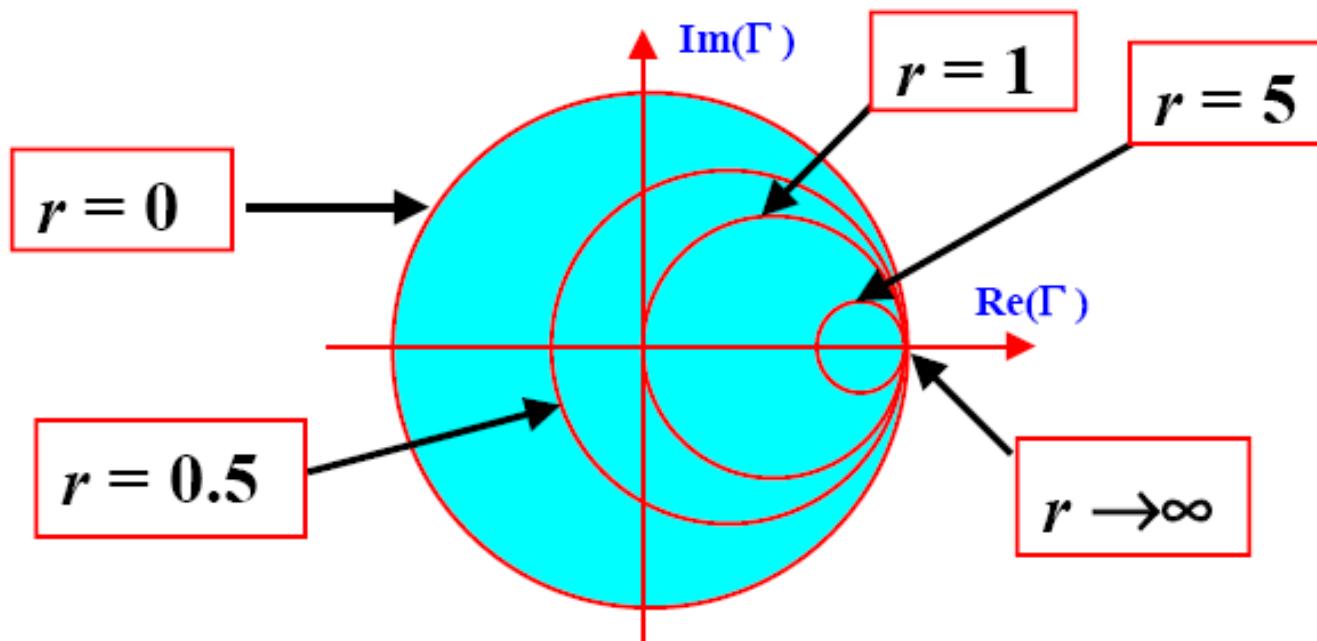
## 2. Smith Chart

$$\left(\text{Re}(\Gamma) - \frac{r}{1+r}\right)^2 + \text{Im}^2(\Gamma) = \left(\frac{1}{1+r}\right)^2 : \text{Resistance circles}$$


Center:  $\left(\frac{r}{1+r}, 0\right)$   
Radius:  $\frac{1}{1+r}$



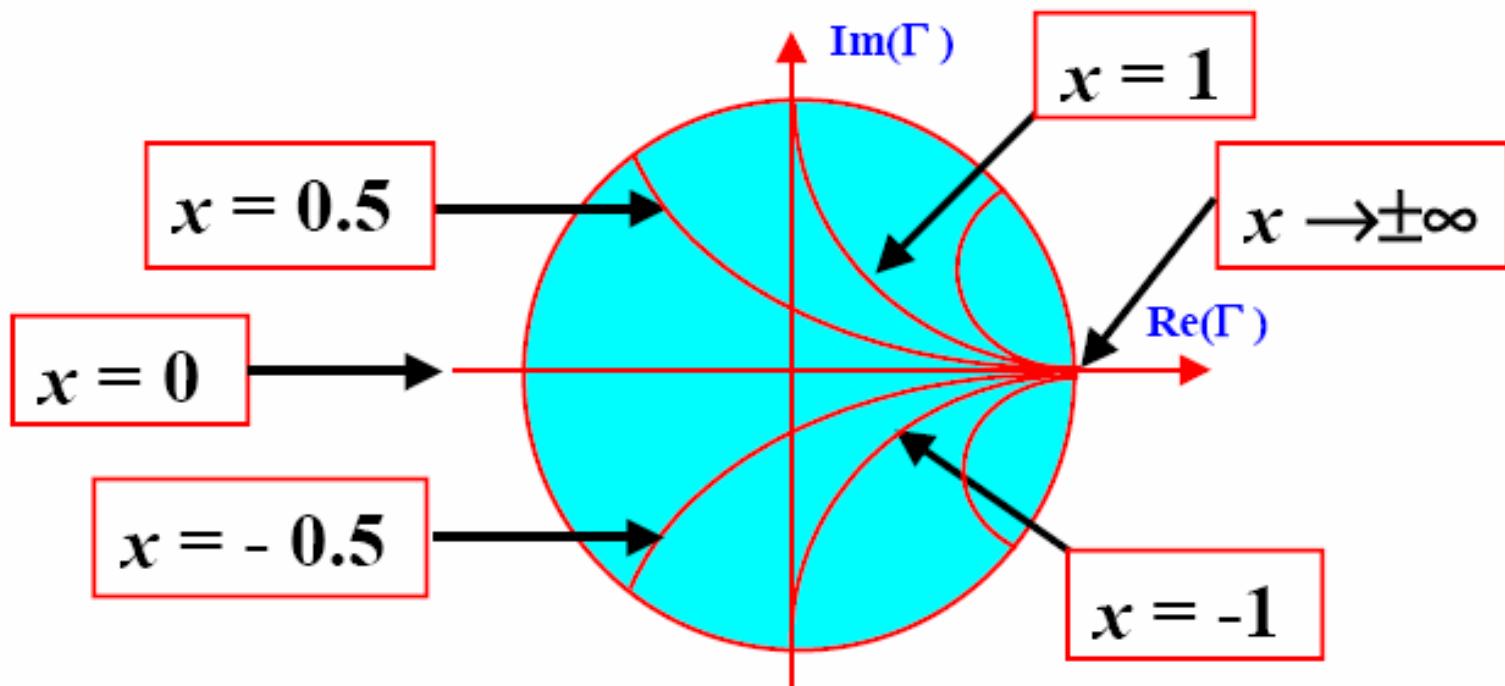
## 2. Smith Chart

$$(\operatorname{Re}(\Gamma) - 1)^2 + \left( \operatorname{Im}(\Gamma) - \frac{1}{x} \right)^2 = \left( \frac{1}{x} \right)^2 : \text{Reactance circles}$$

Center:  $\left( 1, \frac{1}{x} \right)$   
Radius:  $\frac{1}{x}$



# 2. Smith Chart

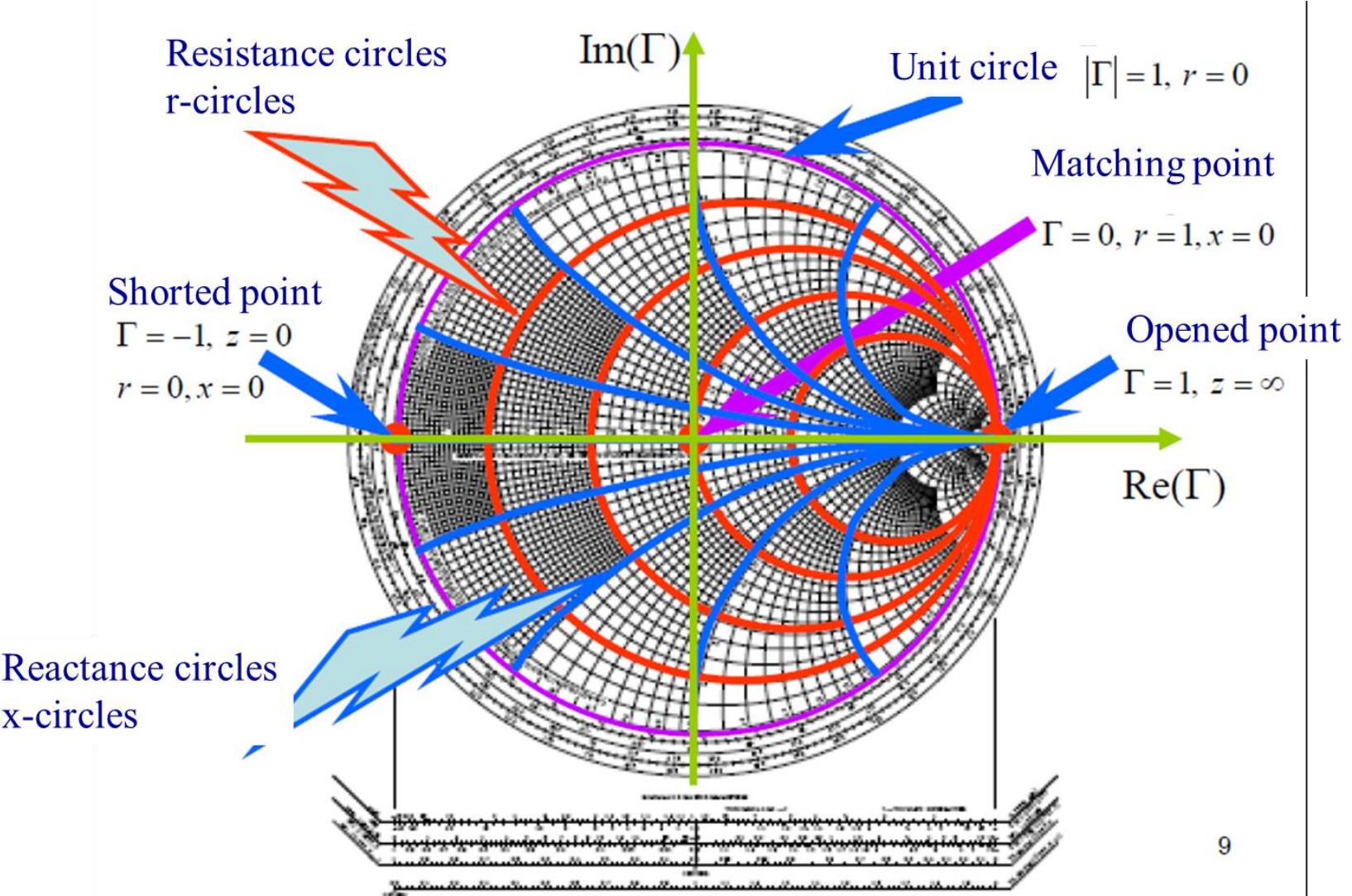


# 2. Smith Chart

**For the constant  $r$  circles:**

1. The centers of all the constant  $r$  circles are on the horizontal axis – real part of the reflection coefficient.
2. The radius of circles decreases when  $r$  increases.
3. All constant  $r$  circles pass through the point  $\Gamma_r = 1, \Gamma_i = 0$ .
4. The normalized resistance  $r = \infty$  is at the point  $\Gamma_r = 1, \Gamma_i = 0$ .

**For the constant  $x$  (partial) circles:**

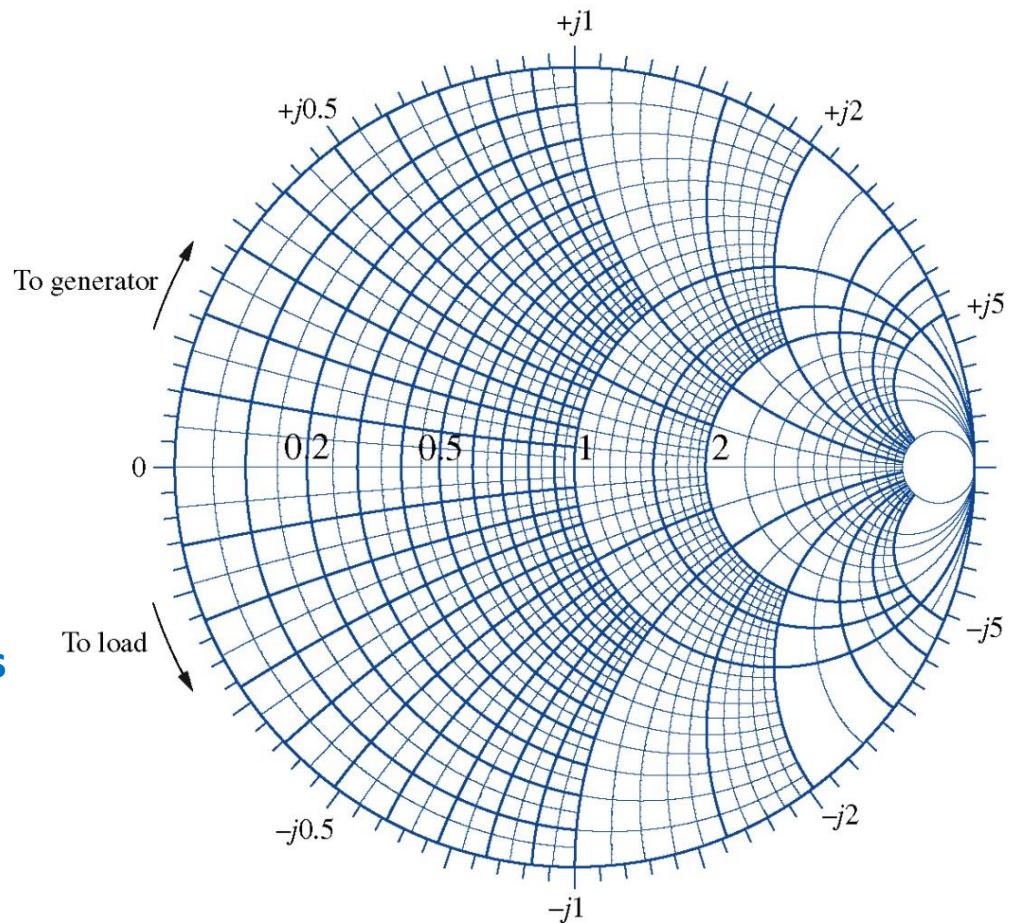
1. The centers of all the constant  $x$  circles are on the  $\Gamma_r = 1$  line. The circles with  $x > 0$  (inductive reactance) are above the  $\Gamma_r$  axis; the circles with  $x < 0$  (capacitive) are below the  $\Gamma_r$  axis.
2. The radius of circles decreases when absolute value of  $x$  increases.
3. The normalized reactances  $x = \pm\infty$  are at the point  $\Gamma_r = 1, \Gamma_i = 0$




# 2. Smith Chart

The Complete Smith Chart


Black Magic Design

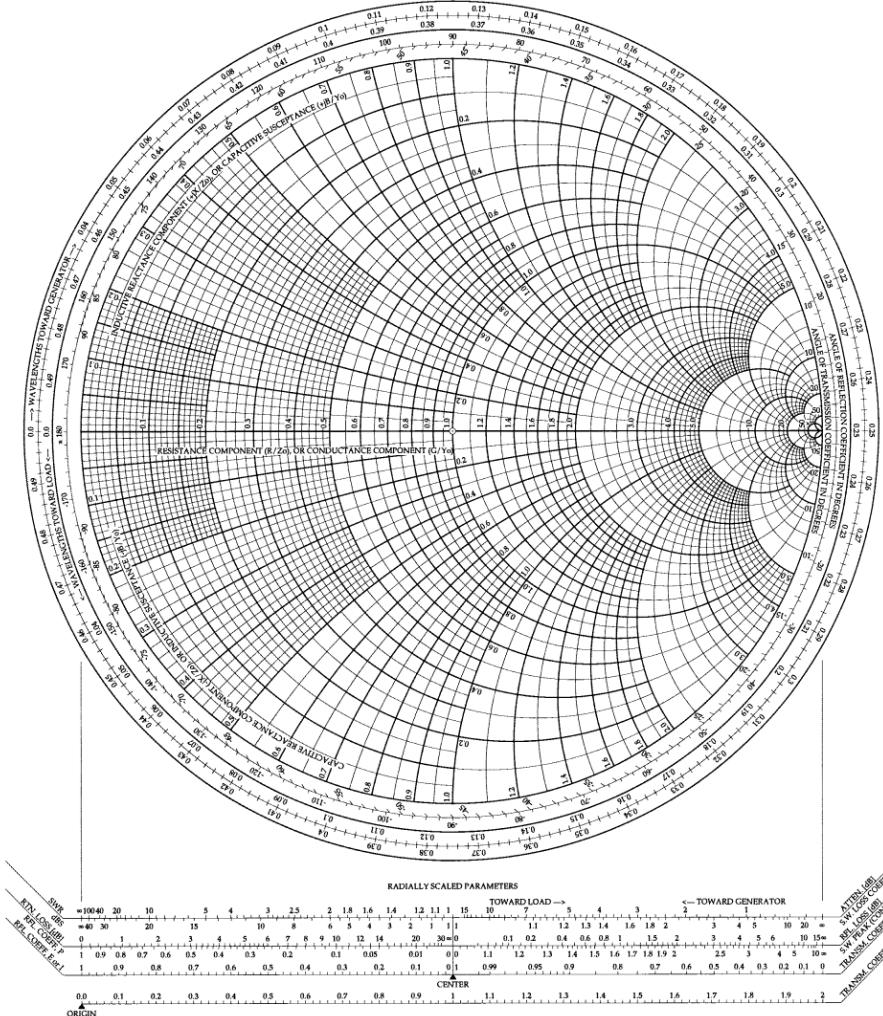


# 2. Smith Chart

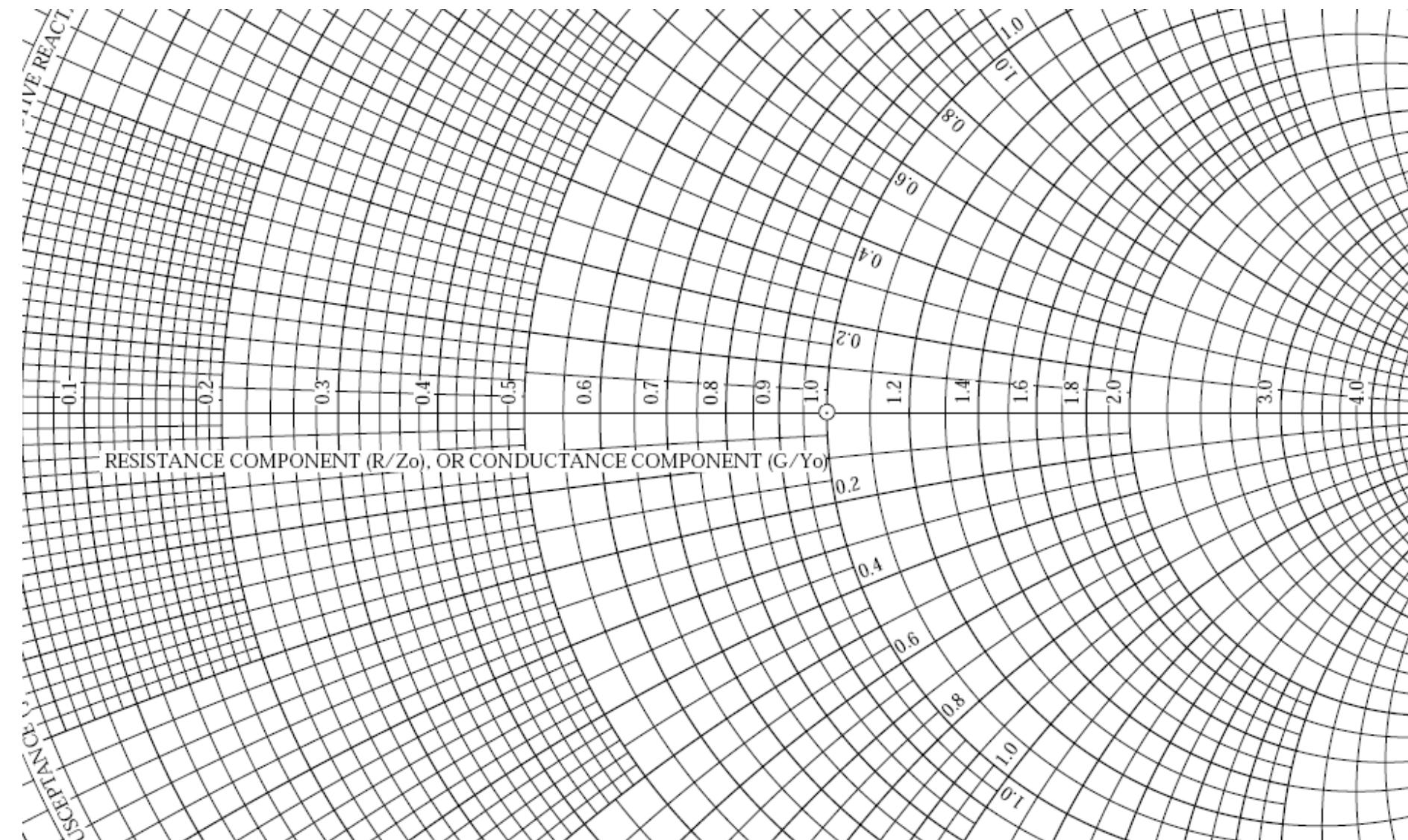

# 2. Smith Chart

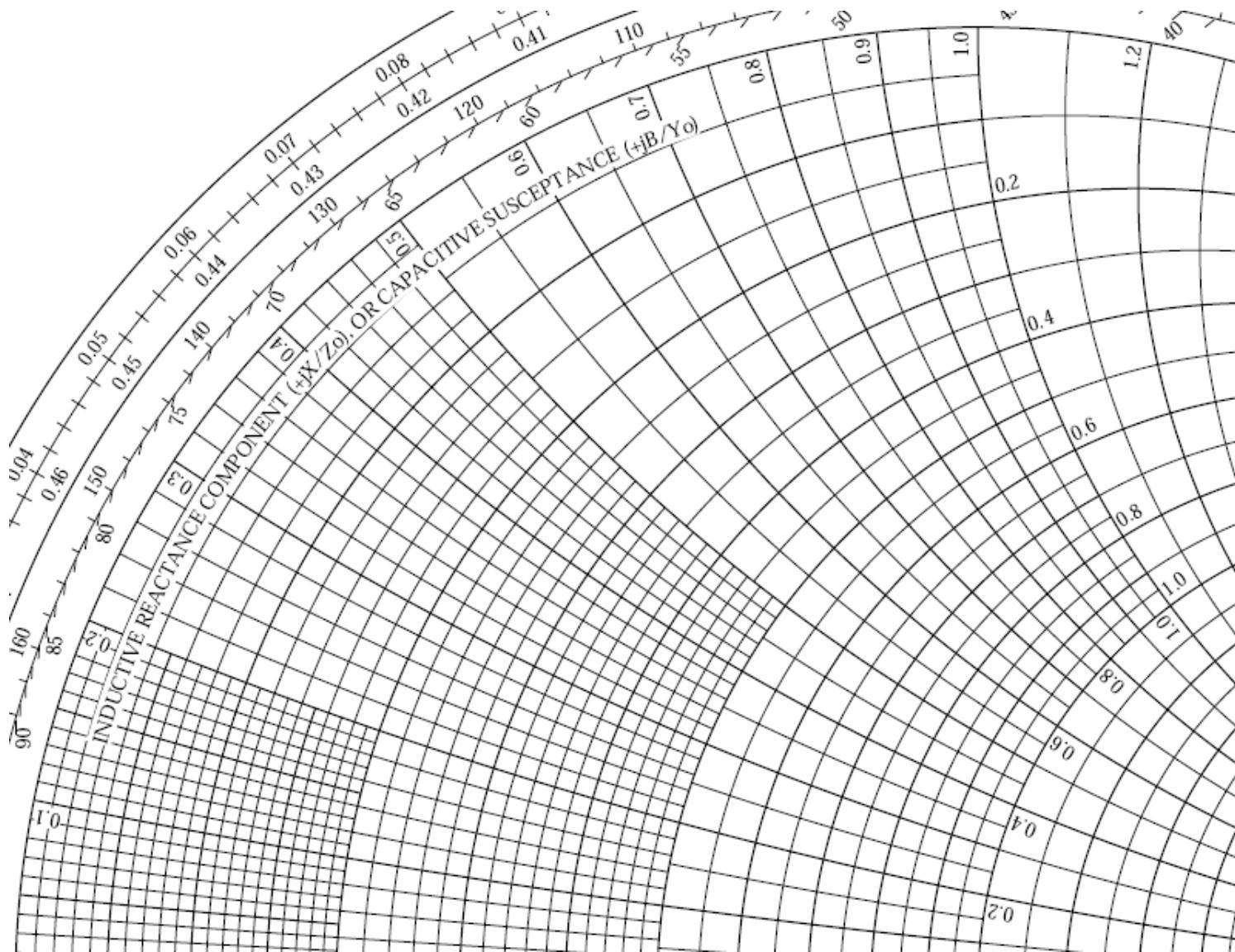


## 2. Smith Chart

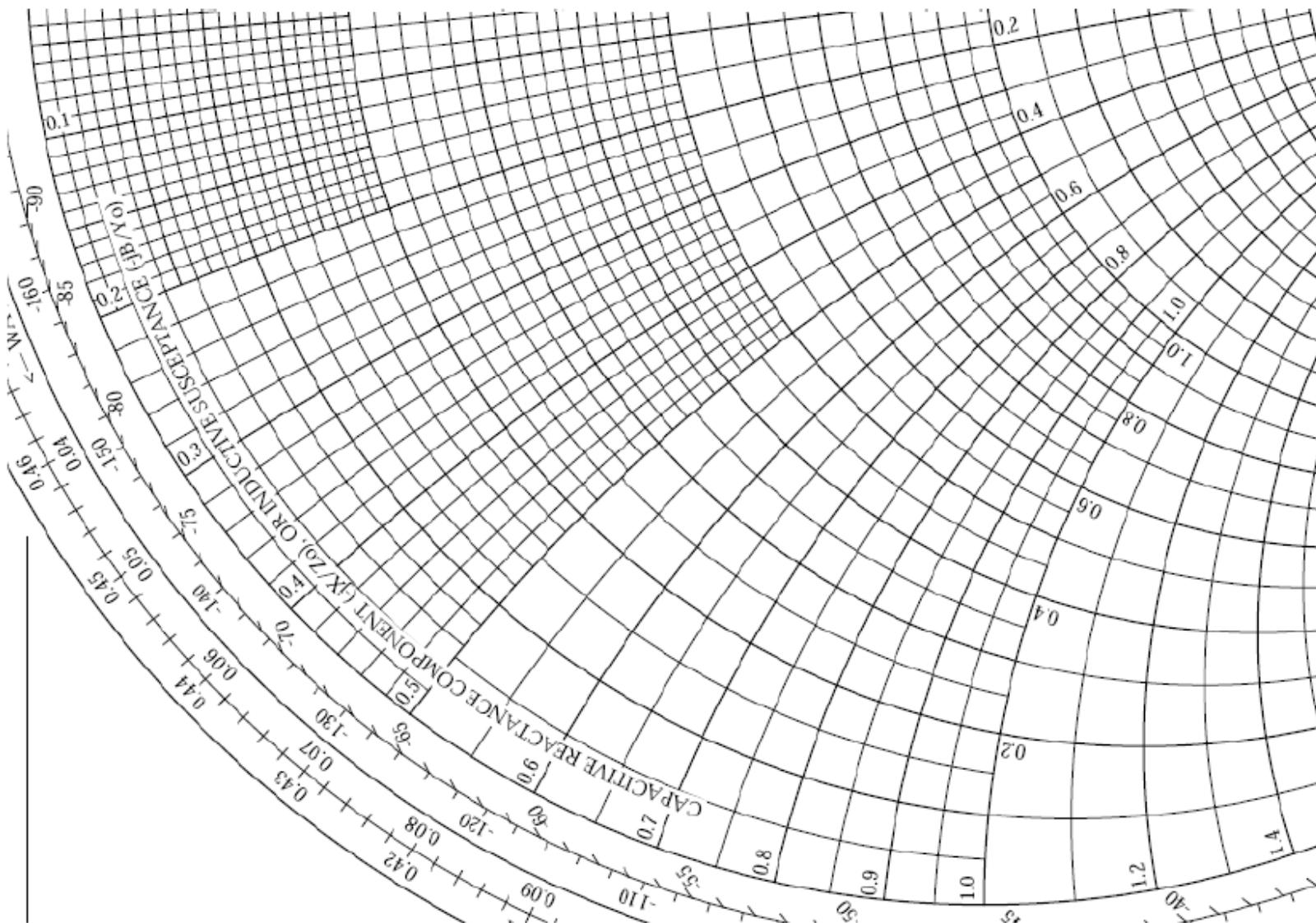


## 2. Smith Chart

$$\Gamma(x) = \Gamma(l) e^{-2\gamma d}$$


Constant  $|\Gamma|$  circle

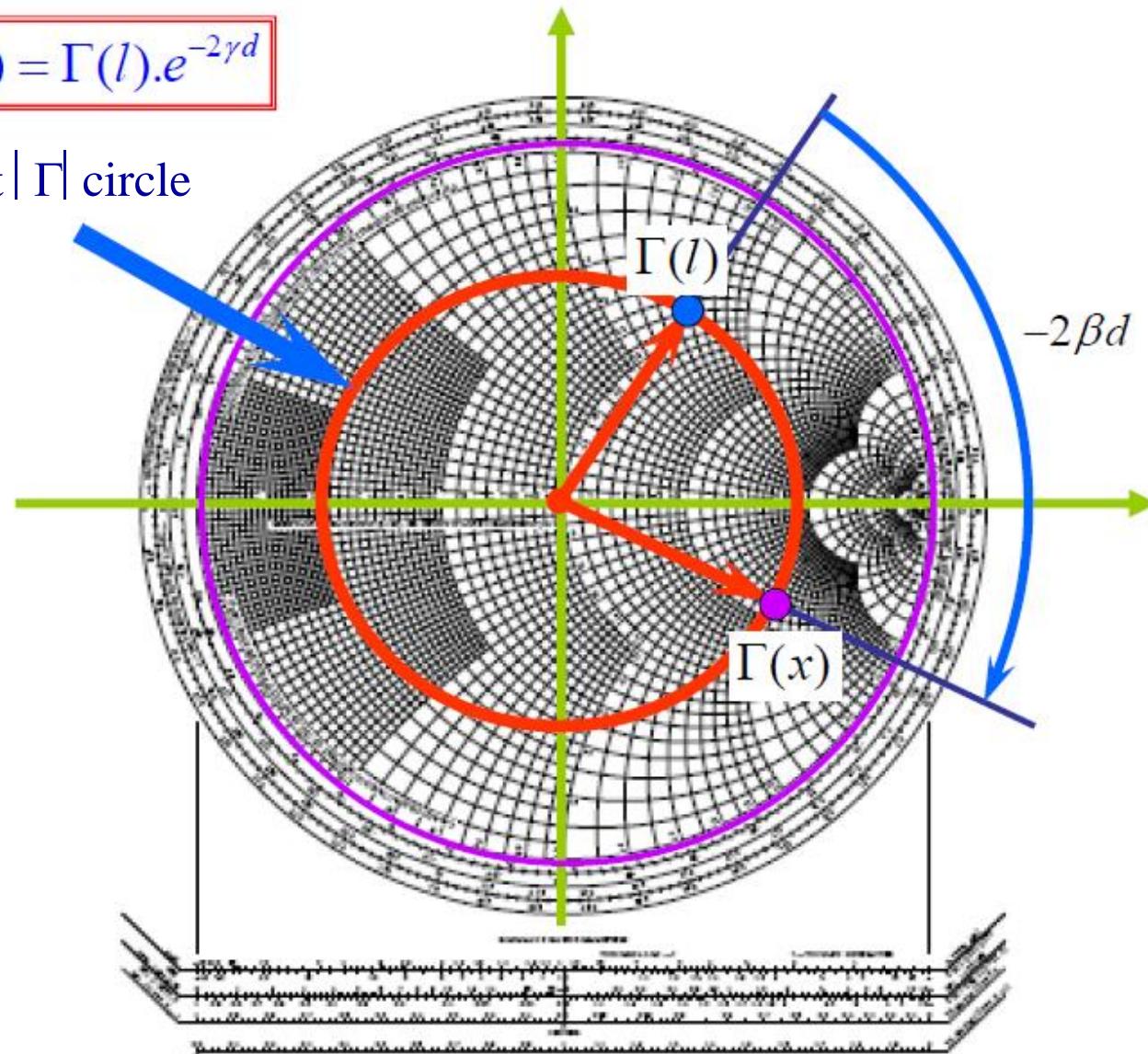


# 2. Smith Chart

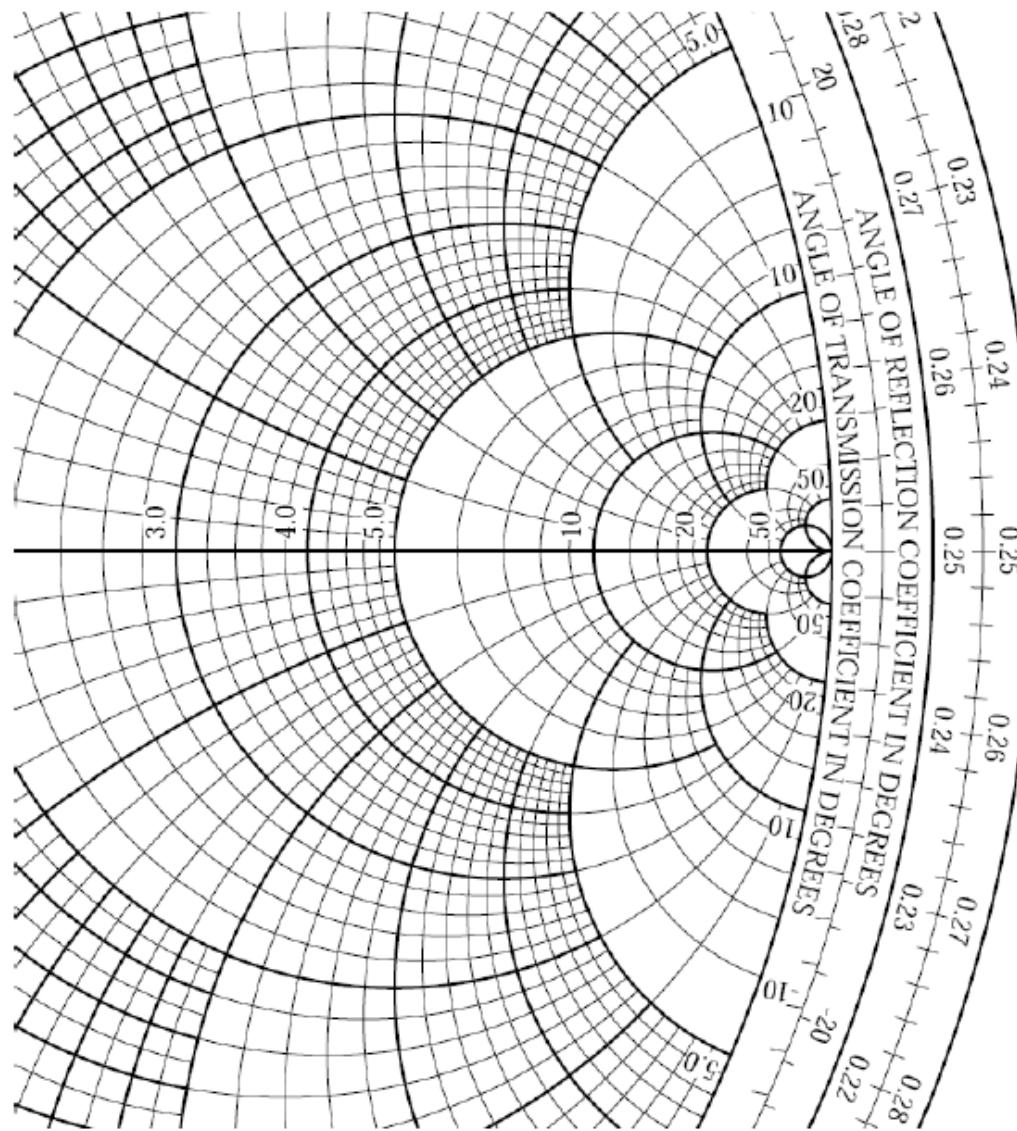

# 2. Smith Chart

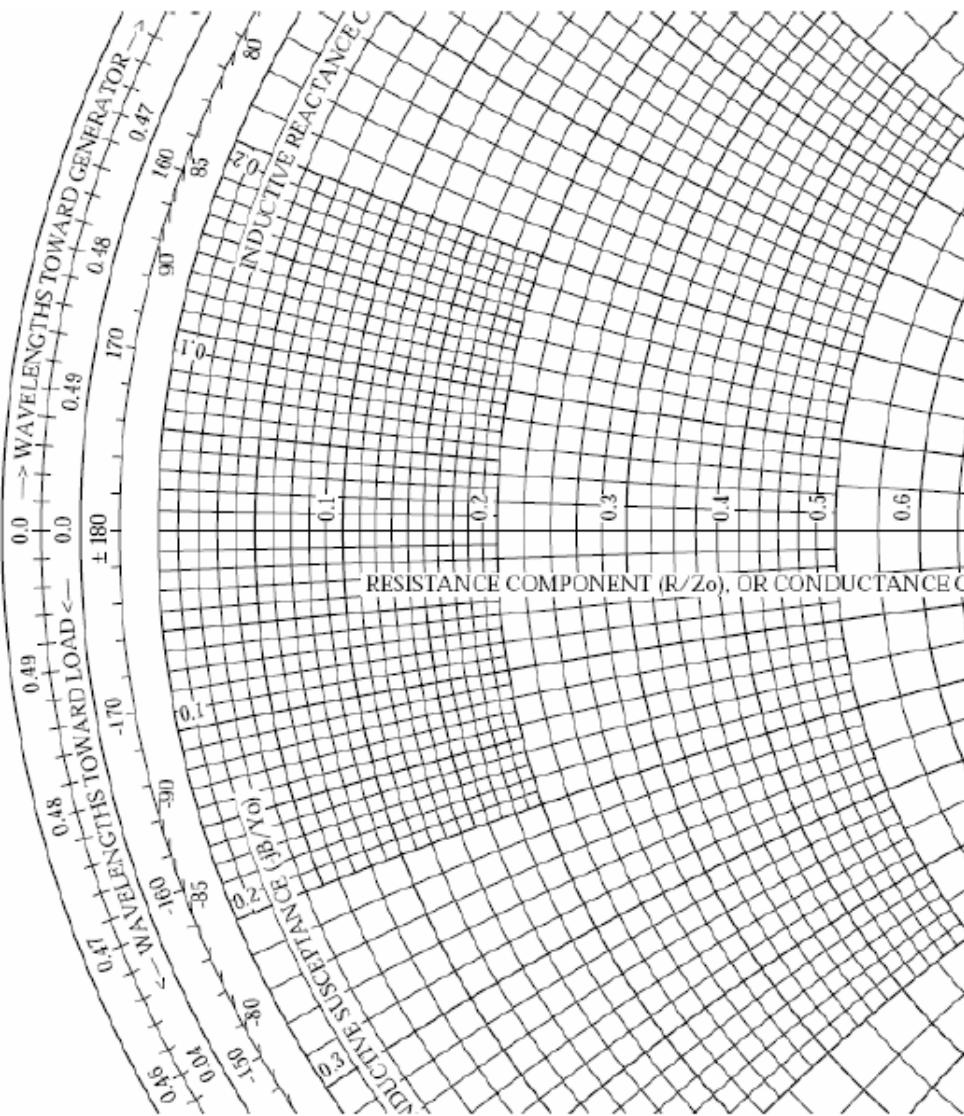

# 2. Smith Chart

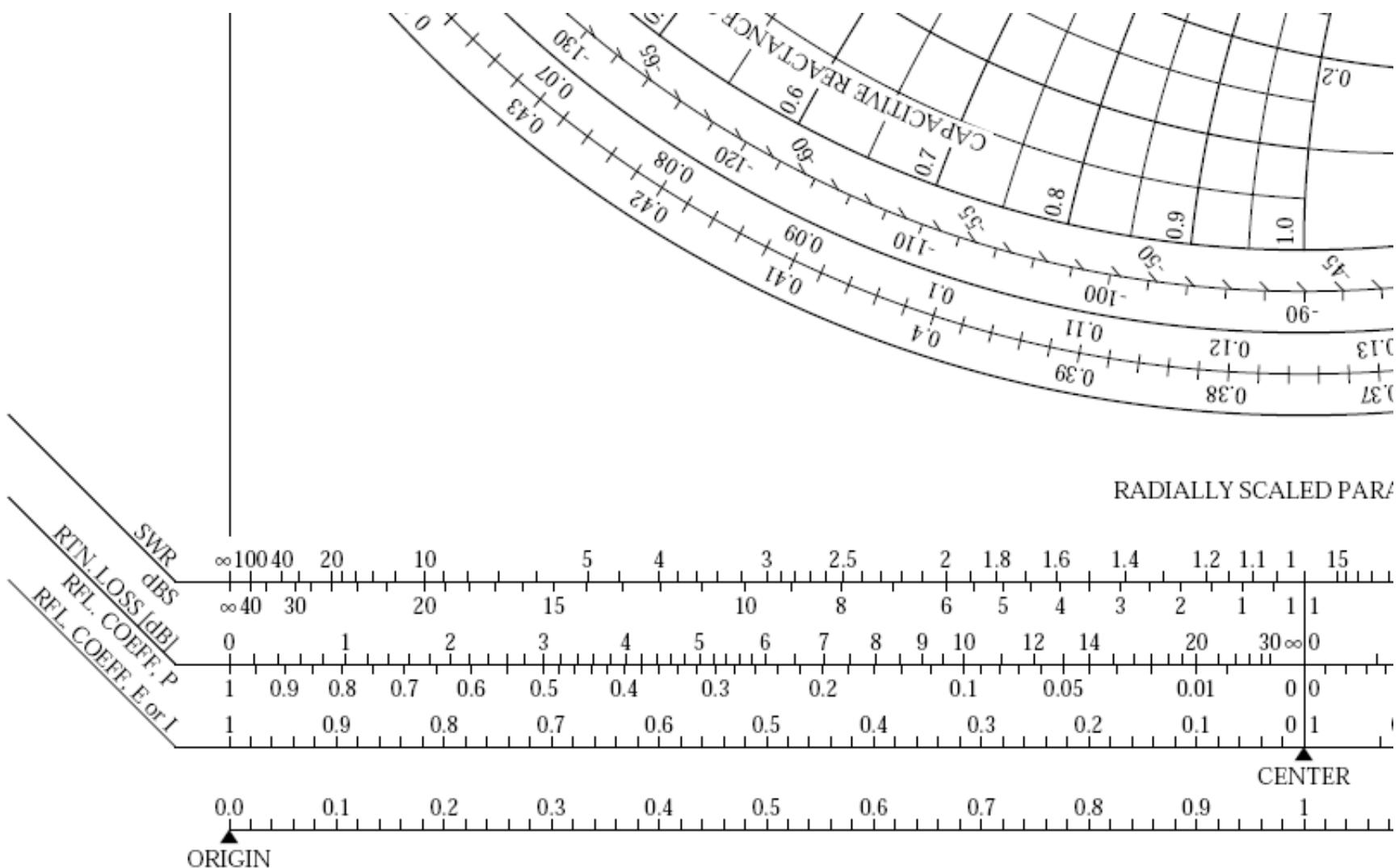

# 3. Smith Chart Applications

- A. Given  $Z(d)$ , find  $\Gamma(d)$       or      Given  $\Gamma(d)$ , find  $Z(d)$ .
- B. Given  $\Gamma_L$  and  $Z_L$ , find  $\Gamma(d)$  and  $Z(d)$ .  
Given  $\Gamma(d)$  and  $Z(d)$ , find  $\Gamma_R$  and  $Z_R$ .
- C. Find  $d_{\max}$  and  $d_{\min}$  (maximum and minimum locations for the VSW pattern).
- D. Find the VSWR.
- E. Given  $Z(d)$ , find  $Y(d)$       or      Given  $Y(d)$ , find  $Z(d)$ .

# 3. Smith Chart Applications

## A. Given $Z(d)$ , find $\Gamma(d)$

1. Normalize the impedance:

$$z(d) = \frac{Z(d)}{Z_0} = \frac{R}{Z_0} + j \frac{X}{Z_0} = r + jx$$

2. Find the circle of constant normalized resistance  $r$ .
3. Find the circle of constant normalized reactance  $x$ .
4. Find the interaction of the two curves indicates the reflection coefficient in the complex plane. The chart provides directly magnitude and the phase angle of  $\Gamma(d)$ .

**Example 1:** Find  $\Gamma(d)$  given  $Z(d) = 25 + j100\Omega$  and  $Z_0 = 50\Omega$

# 3. Smith Chart Applications

1. Normalization

$$\begin{aligned} z(d) &= (25 + j 100)/50 \\ &= 0.5 + j 2.0 \end{aligned}$$

3. Find normalized reactance arc

$$x = 2.0$$

2. Find normalized resistance circle


$$r = 0.5$$

4. This vector represents the reflection coefficient

$$\Gamma(d) = 0.52 + j0.64$$

$$|\Gamma(d)| = 0.8246$$
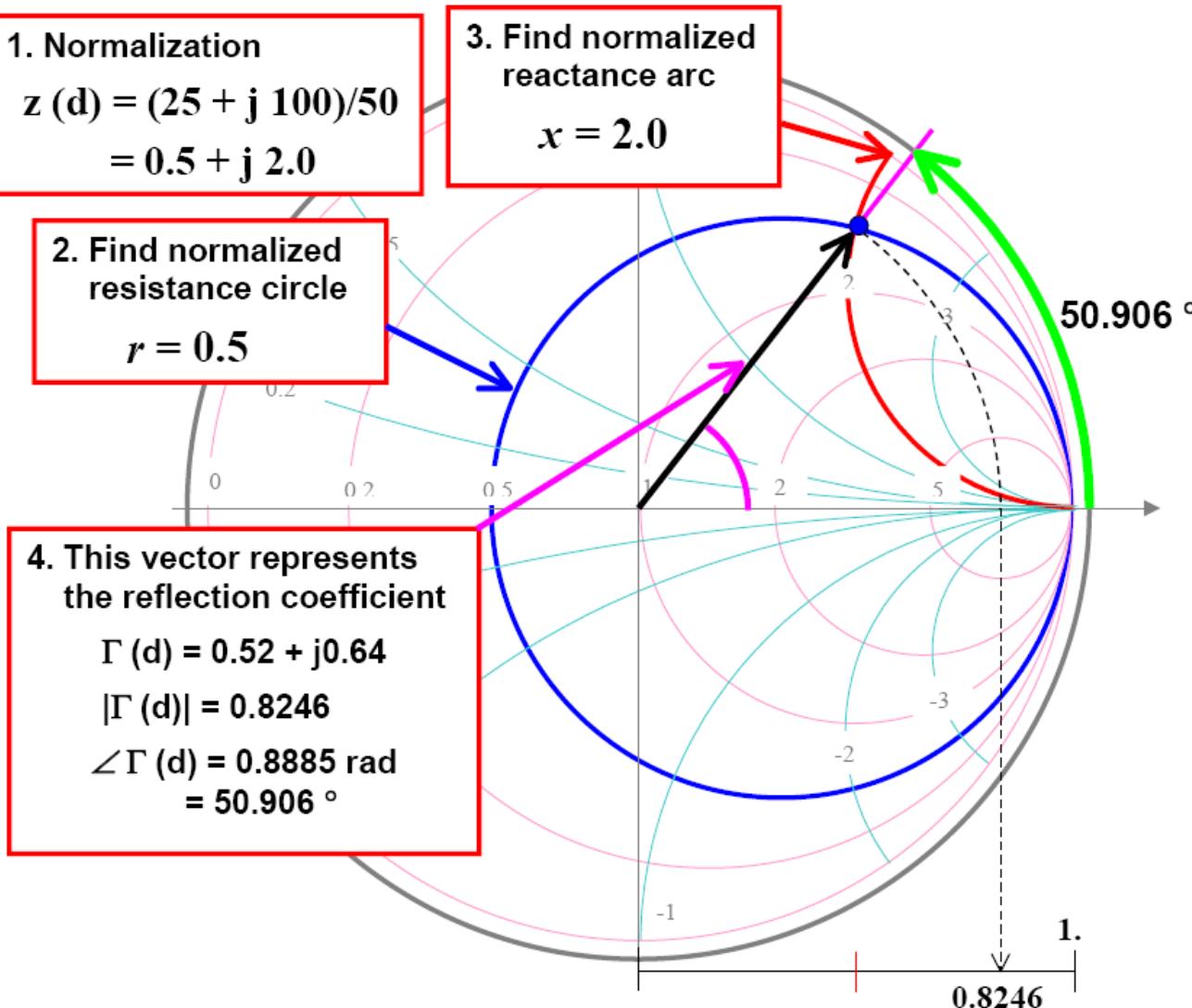
$$\begin{aligned} \angle \Gamma(d) &= 0.8885 \text{ rad} \\ &= 50.906^\circ \end{aligned}$$



# 3. Smith Chart Applications

## A. Given $\Gamma(d)$ , find $Z(d)$

1. Determine the complex point representing the given reflection coefficient  $\Gamma(d)$  on the chart.
2. Read the value of normalized resistance  $r$  and the normalized reactance  $x$  that correspond to the reflection coefficient point.
3. The normalized impedance is:  $z(d) = r + jx$
4. The actual impedance is:  $Z(d) = z(d)Z_0$

# 3. Smith Chart Applications

## B. Given $\Gamma_L$ and $Z_L$ , find $\Gamma(d)$ and $Z(d)$


The magnitude of the reflection coefficient is constant along a lossless T.L. terminated by a specific load, since:

$$|\Gamma(d)| = |\Gamma_L e^{-j2\beta d}| = |\Gamma_L|$$

1. Identify the load reflection coefficient  $\Gamma_L$  and the normalized load impedance  $Z_L$  on the Smith Chart.
2. Draw the circle of constant coefficient amplitude  $|\Gamma(d)| = |\Gamma_L|$
3. Starting from the point representing the load, travel on the circle in the *clockwise* direction by an angle  $\theta = 2\beta d$ .
4. The new location on the chart corresponds to location  $d$  on the T.L. Here the value of  $\Gamma(d)$  and  $Z(d)$  can be read from the chart.


**Example:** Find  $\Gamma(d)$  and  $Z(d)$  given  $Z_L = 25 + j100\Omega$ ,  $Z_0 = 50\Omega$  and  $d = 0.18\lambda$

# 3. Smith Chart Applications

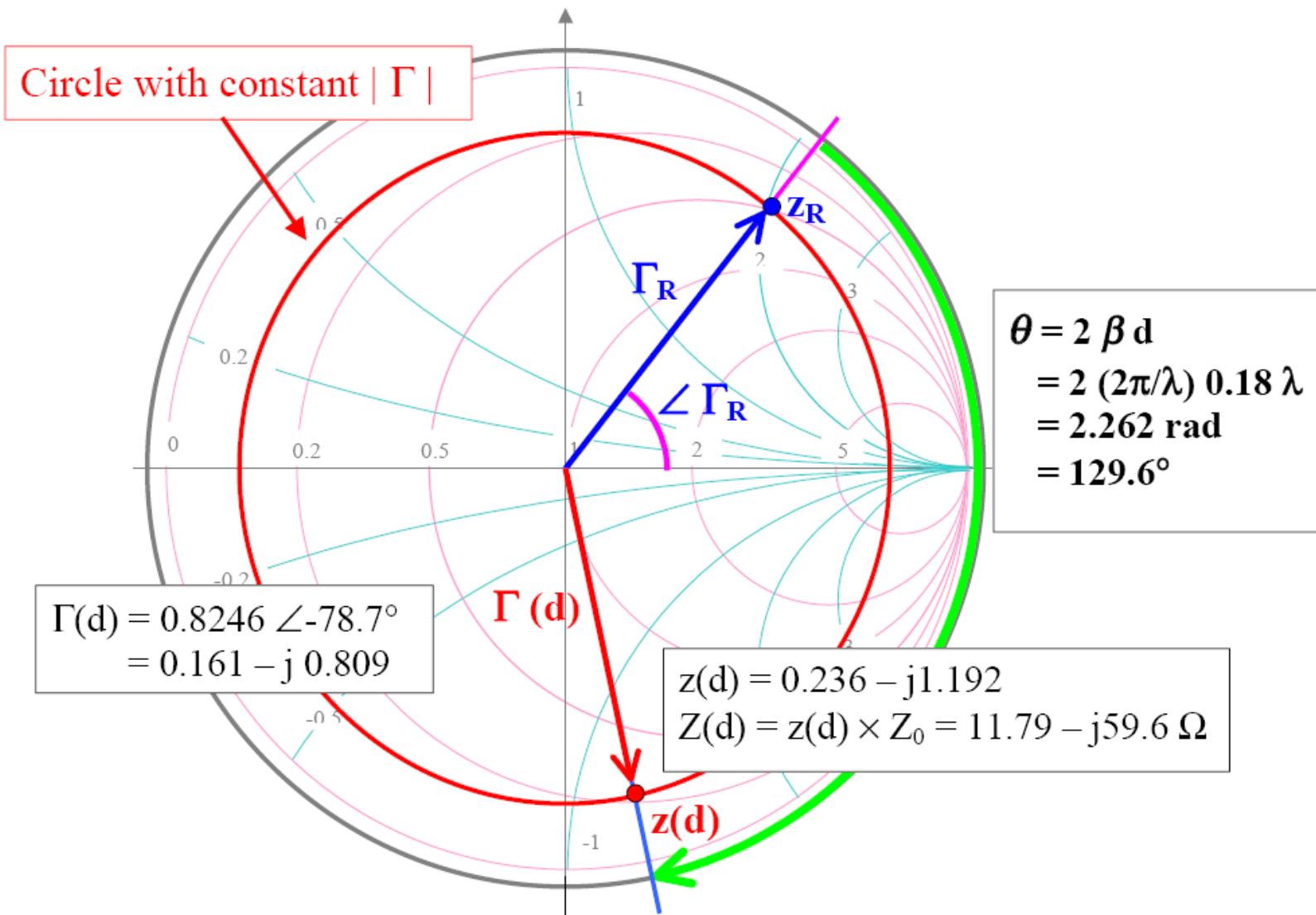

# 3. Smith Chart Applications

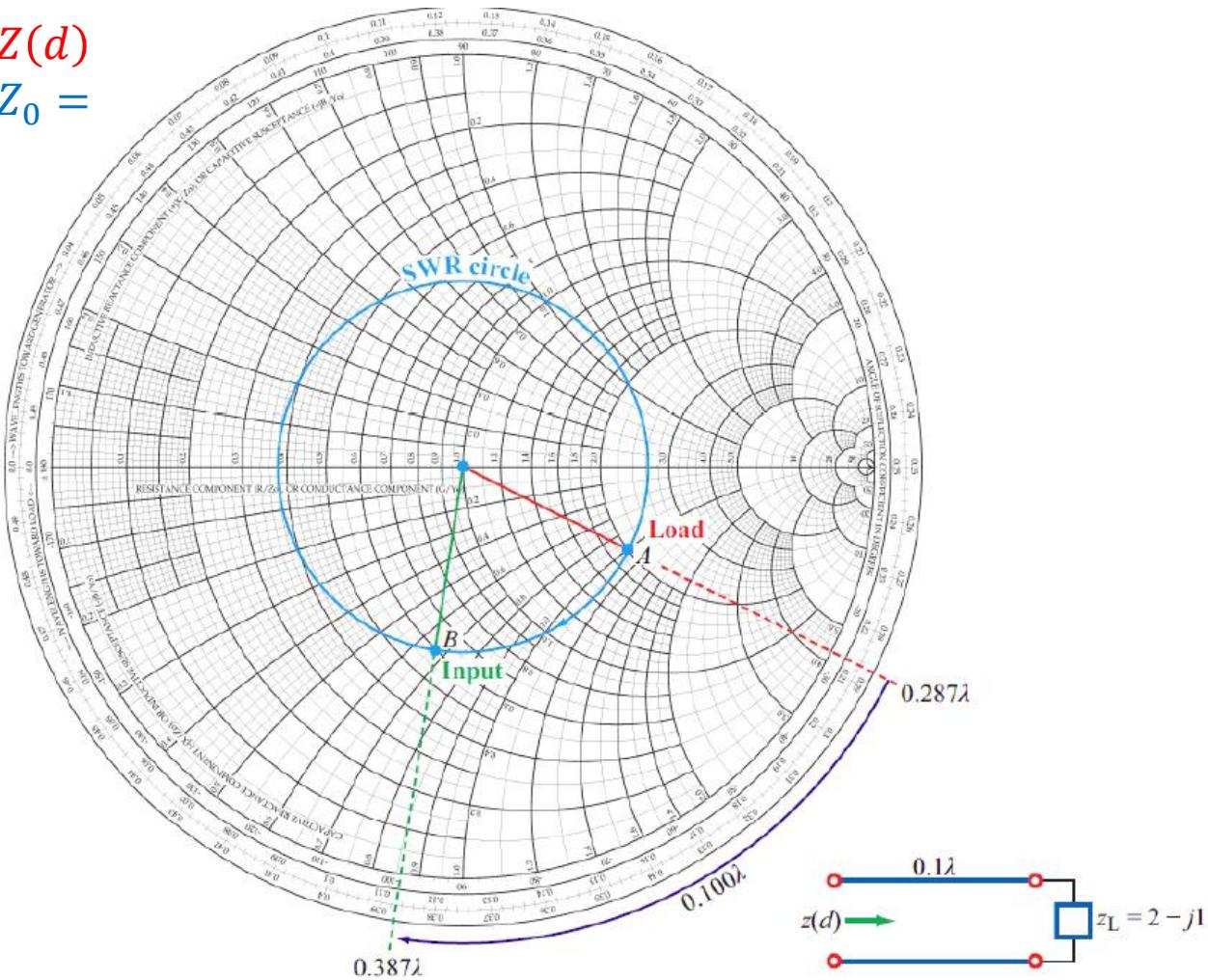**Example 3:** Find  $\Gamma(d)$  and  $Z(d)$  given  $Z_R = 100 - j50\Omega$ ,  $Z_0 = 50\Omega$  and  $d = 0.1\lambda$




# 3. Smith Chart Applications

## C. Given $\Gamma_L$ and $Z_L$ , find $d_{max}$ and $d_{min}$

1. Identify the load reflection coefficient  $\Gamma_L$  and the normalized load impedance  $Z_L$  on the Smith Chart.
2. Draw the circle of constant coefficient amplitude  $|\Gamma(d)| = |\Gamma_L|$
3. The circle intersects the real axis of the reflection coefficient at two points which identify  $d_{max}$  (when  $\Gamma(d) = \text{real positive}$ ) and  $d_{min}$  (when  $\Gamma(d) = \text{real negative}$ ).
4. The Smith chart provides an outer graduation where the distances normalized to the wavelength can be read directly.

**Example 4:** Find  $d_{max}$  and  $d_{min}$  for  $Z_L = 100 + j50\Omega$ ,  $Z_0 = 50\Omega$  and  $d = 0.18\lambda$

# 3. Smith Chart Applications

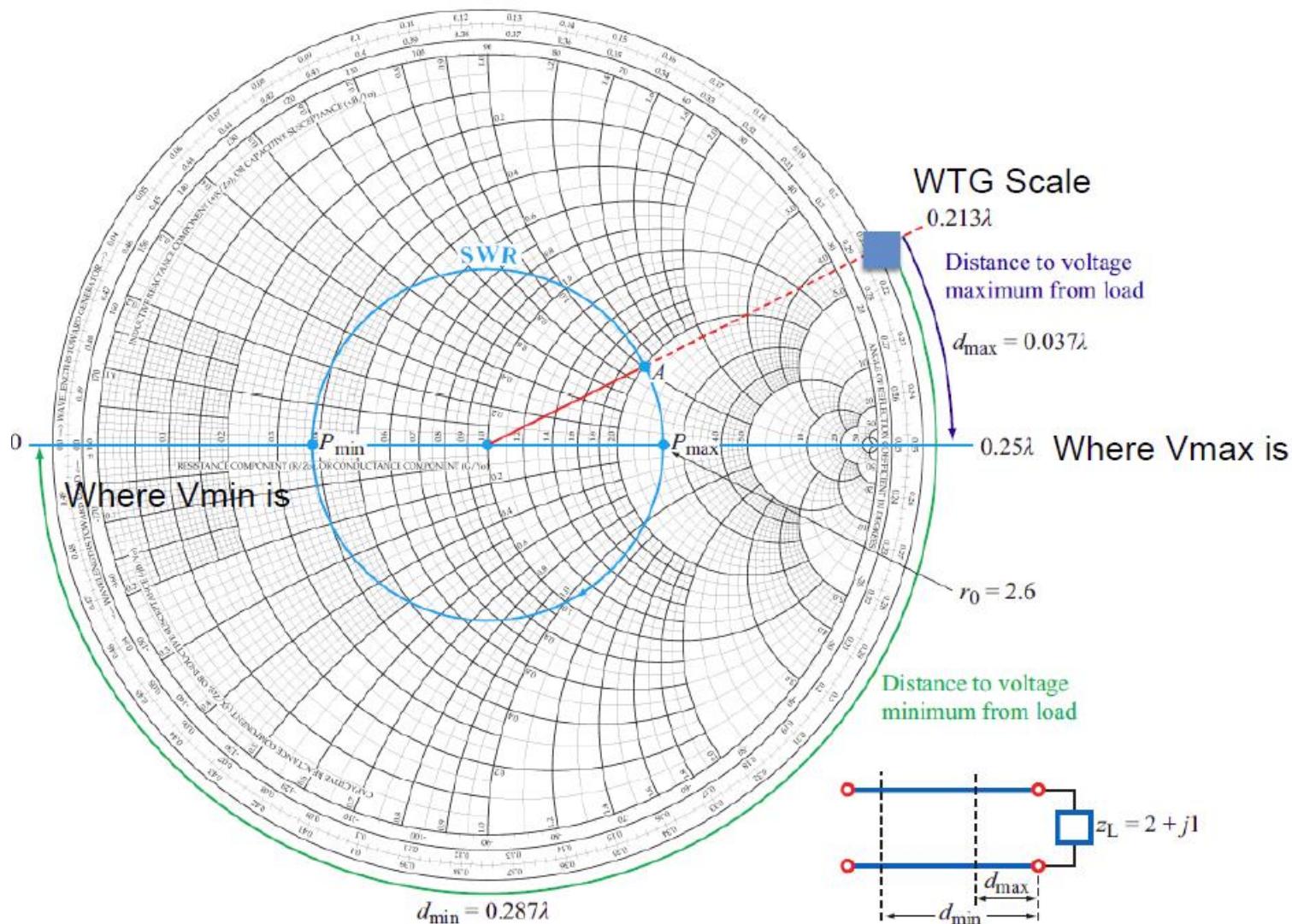

# 3. Smith Chart Applications

## D. Given $\Gamma_L$ and $Z_L$ , find VSWR

The VSWR is defined as:  $VSWR = \frac{V_{max}}{V_{min}} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|}$

The normalized impedance at the maximum location of the SW pattern is given by:

$$z(d_{max}) = \frac{1 + \Gamma(d_{max})}{1 - \Gamma(d_{max})} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} = VSWR$$

This quantity is always real and greater than 1. The VSWR is simply obtained on the Smith Chart by reading the value of real normalized impedance at the location  $d_{max}$  where  $\Gamma$  is real and positive.

**Example 5:** Find VSWR for  $Z_L = 25 \pm j100\Omega$ ,  $Z_0 = 50\Omega$ .

# 3. Smith Chart Applications

## E. Given $Z(d)$ , find $Y(d)$

- ❖ The normalized impedance and admittance are defined as:

$$z(d) = \frac{1 + \Gamma(d)}{1 - \Gamma(d)} \quad y(d) = \frac{1 - \Gamma(d)}{1 + \Gamma(d)}$$


- ❖ Since:  $\Gamma\left(d + \frac{\lambda}{4}\right) = -\Gamma(d) \rightarrow z\left(d + \frac{\lambda}{4}\right) = y(d)$

- ❖ The actual values are given by:

$$Z\left(d + \frac{\lambda}{4}\right) = Z_0 z\left(d + \frac{\lambda}{4}\right) \quad Y\left(d + \frac{\lambda}{4}\right) = Y_0 y\left(d + \frac{\lambda}{4}\right) = \frac{y\left(d + \frac{\lambda}{4}\right)}{Z_0}$$

**Example 6:** Find  $Y_L$  given  $Z_L = 25 \pm j100\Omega$ ,  $Z_0 = 50\Omega$ .

# 3. Smith Chart Applications

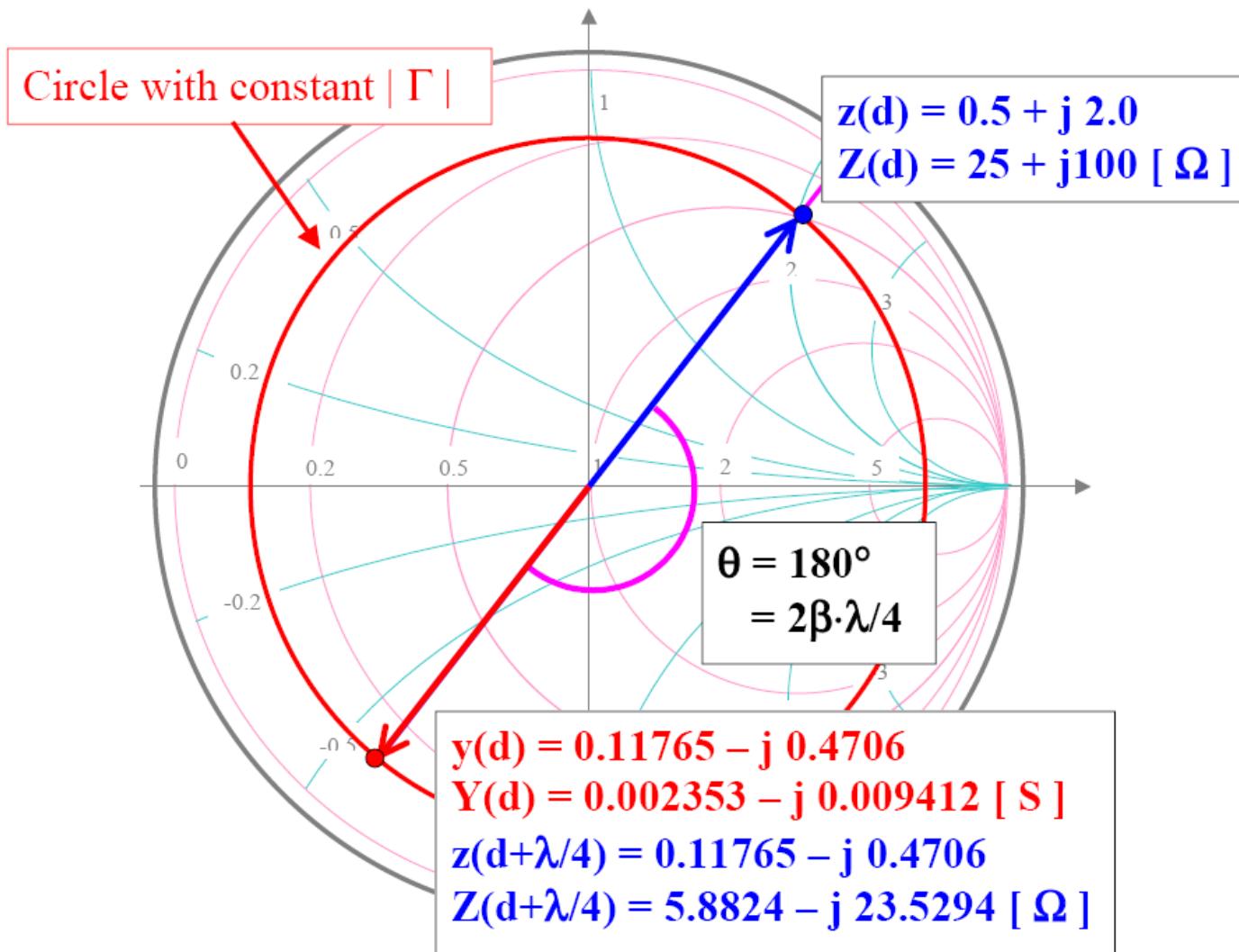


# 3. Smith Chart: Y Smith Chart

- The reflection coefficient is written as:


$$\Gamma = \frac{z - 1}{z + 1} = \frac{\frac{1}{y} - 1}{\frac{1}{y} + 1} = -\frac{y - 1}{y + 1}$$

$$\Gamma = \frac{z - 1}{z + 1} : Z \text{ Smith Chart}$$
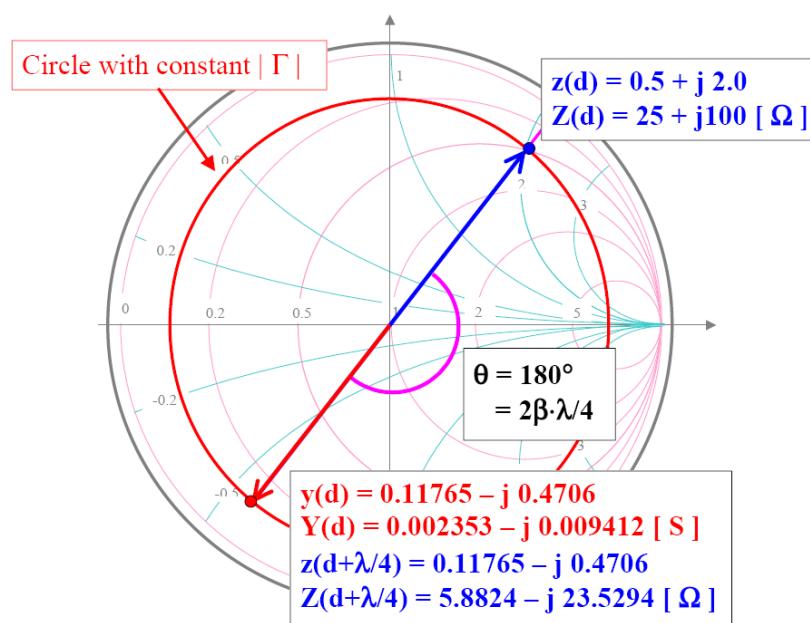
$$-\Gamma = \frac{y - 1}{y + 1} : Y \text{ Smith Chart}$$



Smith Chart for Admittances

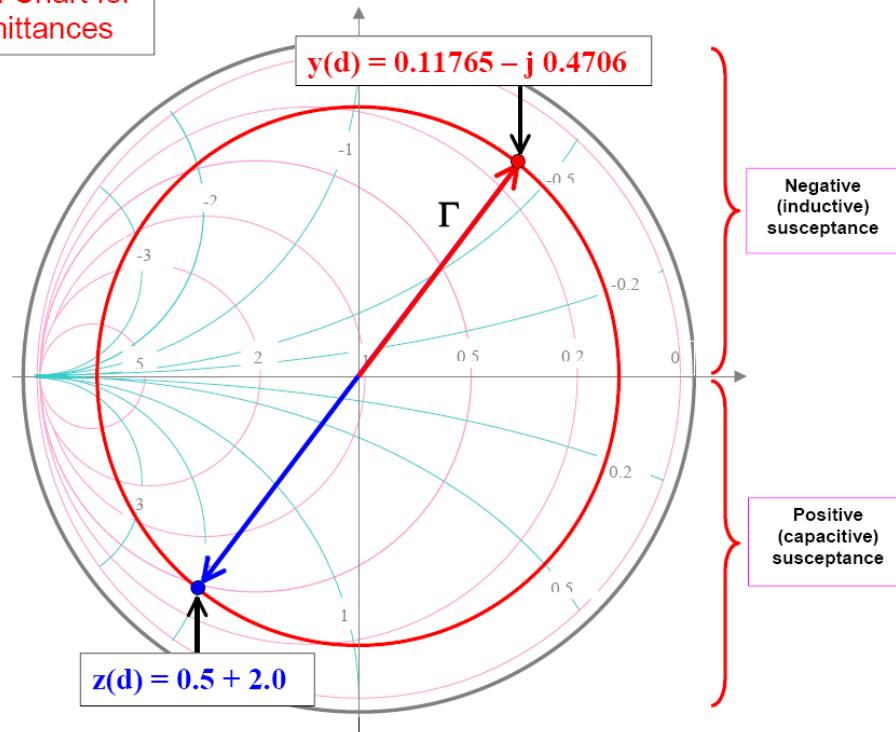

# 3. Smith Chart: Y Smith Chart

$$\Gamma = \frac{z - 1}{z + 1} : Z \text{ Smith Chart}$$


$$-\Gamma = \frac{y - 1}{y + 1} : Y \text{ Smith Chart}$$

- ❖ Since related impedance and admittance are on opposite sides of the same Smith Chart, the imaginary parts always have different sign.  
Numerically we have:

$$z = r + jx \quad y = g + jb = \frac{1}{z}$$



$$g = \frac{r}{r^2 + x^2}$$

$$b = -\frac{x}{r^2 + x^2}$$

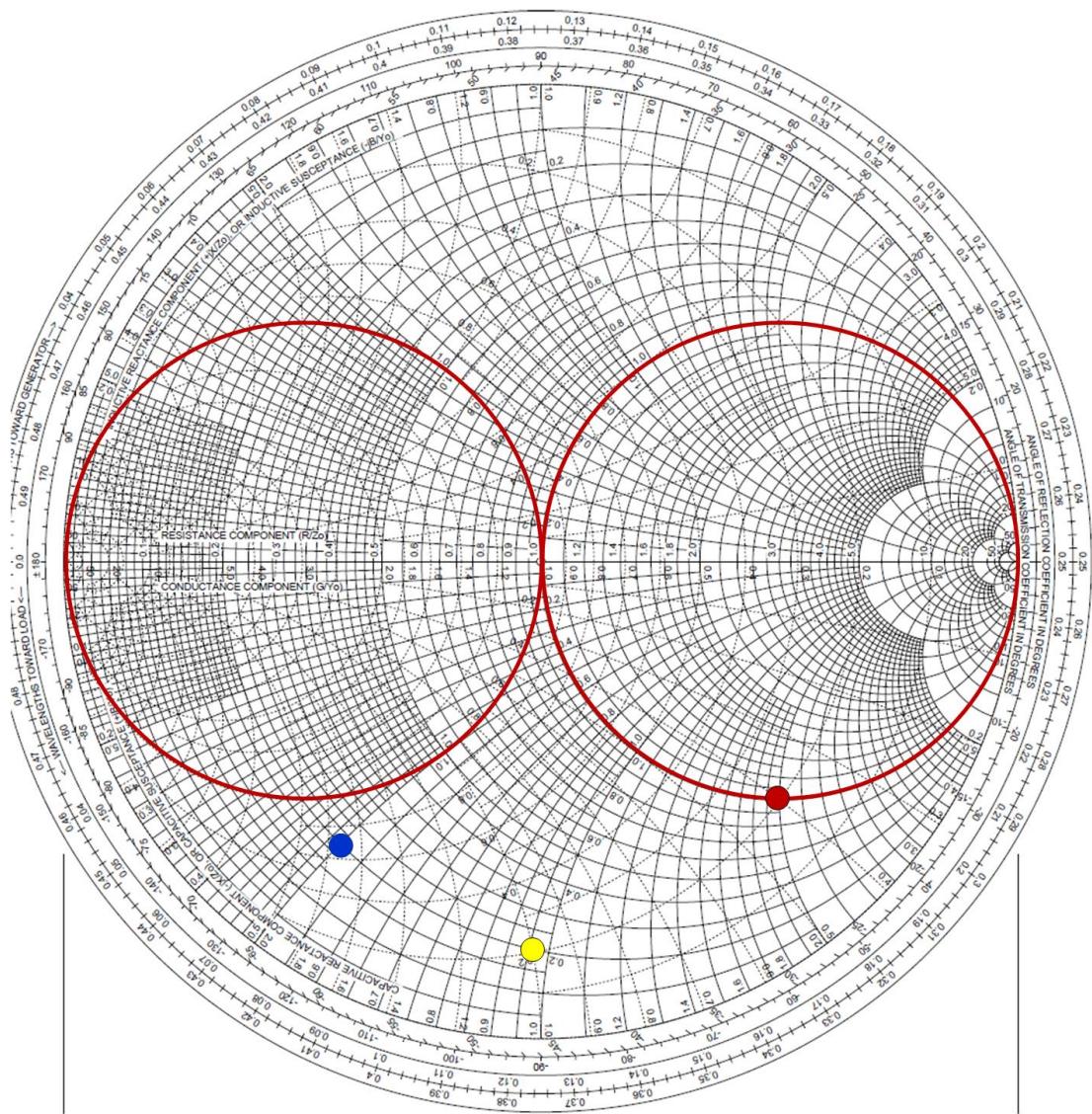

# 3. Smith Chart Applications

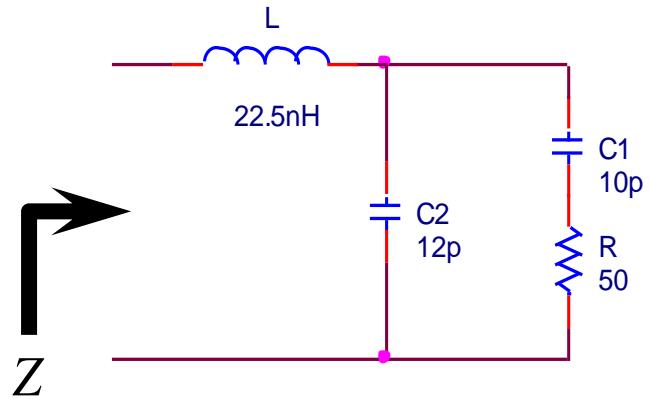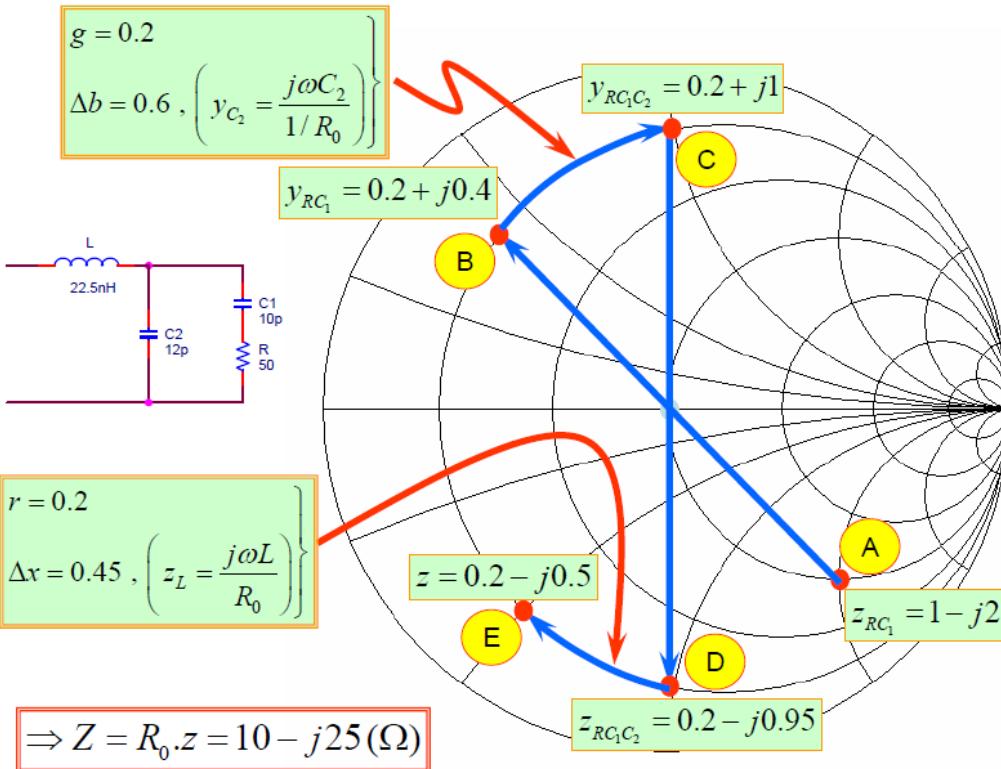
**Example 7:** Find impedance of a complex circuit using Smith Chart where  $R_0 = 50\Omega$  and  $\varpi = 10^9 \text{ rad/s}$ .



$$z_{RC_1} = \frac{R + 1/j\varpi C_1}{R_0} = 1 - j2$$

# 3. Smith Chart Applications


**More convenient ?**

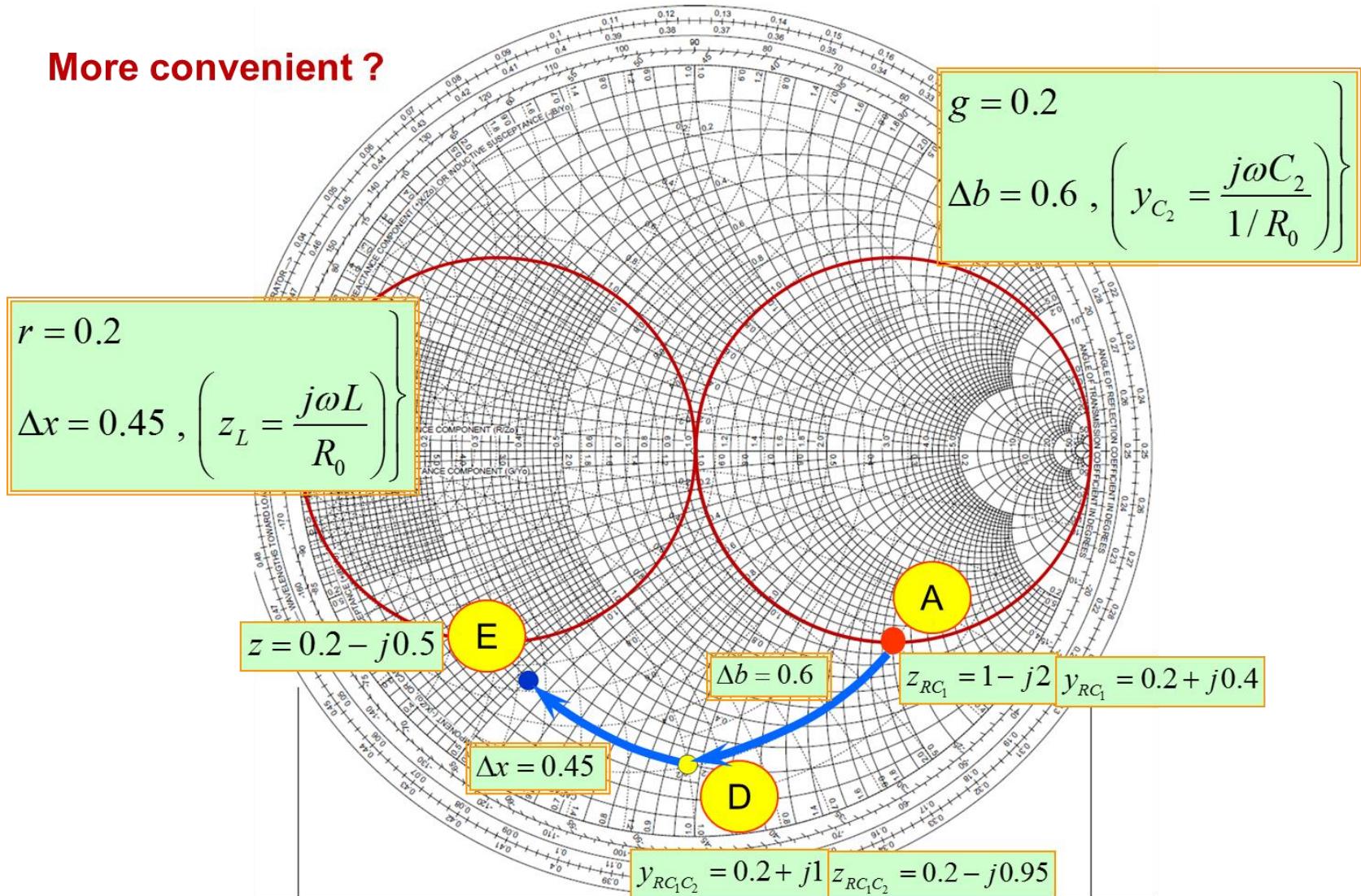

# 3. Smith Chart Applications

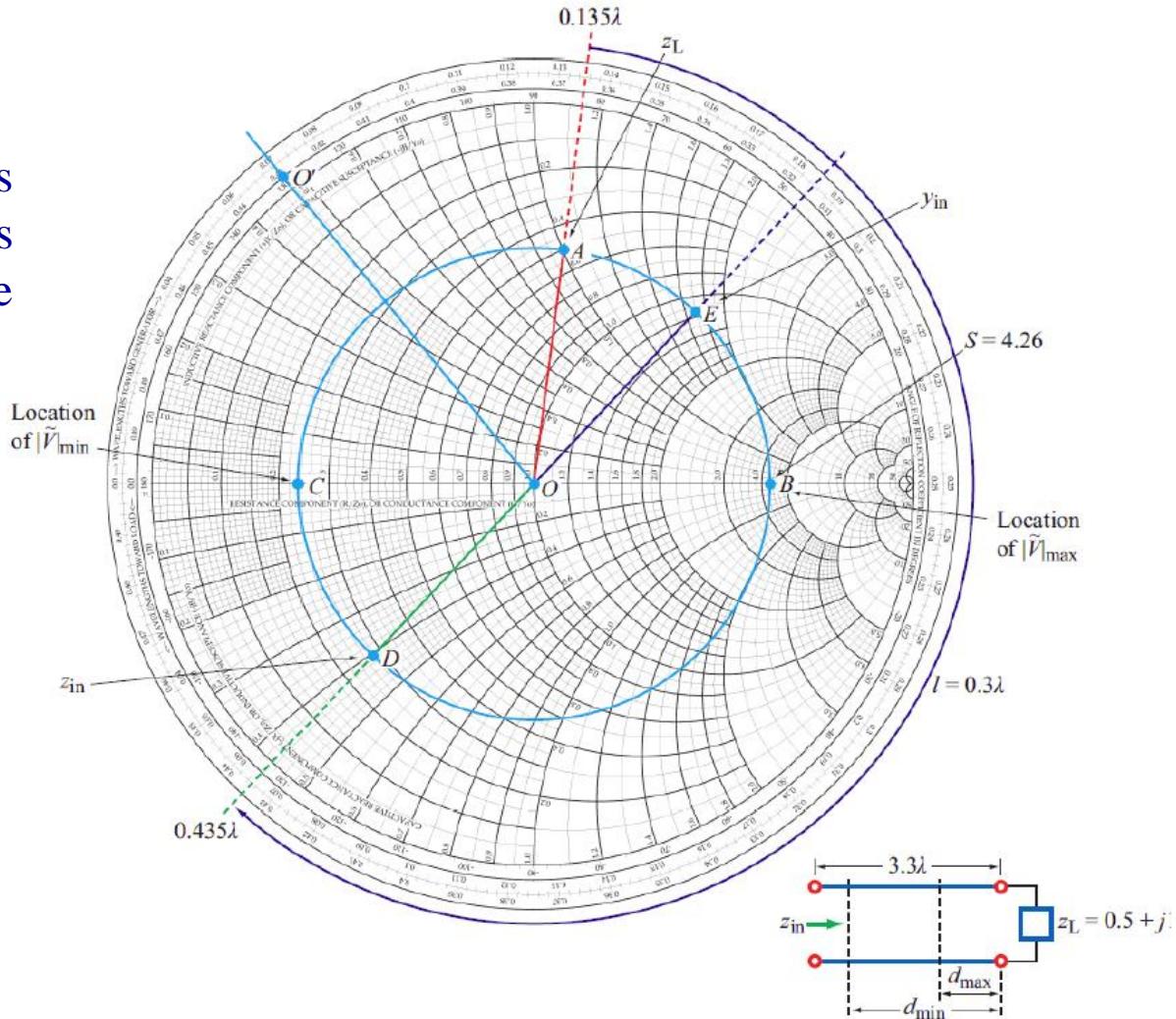**Example 8:** A  $50\Omega$  lossless T.L. of length  $3.3\lambda$  is terminated by a load impedance  $Z_L = (25 + j50)\Omega$ .


- Find  $\Gamma$ .
- Find VSWR.
- Find  $d_{\max}$  and  $d_{\min}$ .
- Find  $Z_{in}$  of T.L.
- Find  $Y_{in}$ .



# 4. Impedance Matching

## Maximum power transfer

## Impedance Matching

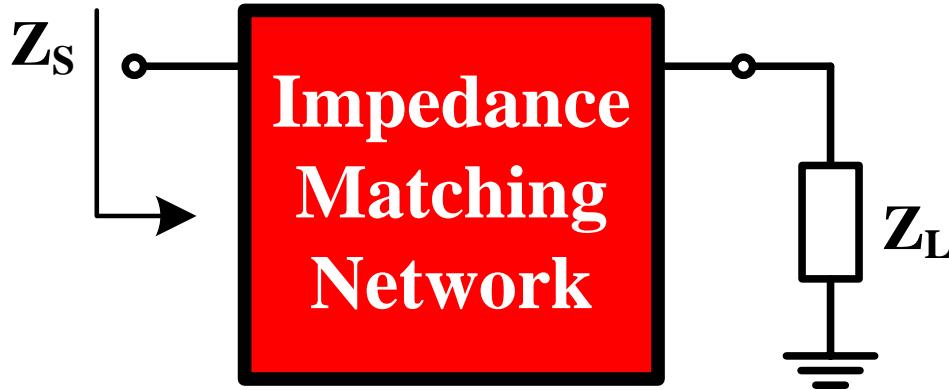

## What are Applications ?







- ❖ T.L.
- ❖ Amplifier Design PA, LNA
- ❖ Component Design
- ❖ Equipment Interfaces

- ❖ Using lump elements
- ❖ Using transmission lines
- ❖ ADS Smith Chart tool

- ❖ Matching with Lumped Elements
- ❖ Single-Stub Matching Networks
- ❖ Quarter-wave Transformer

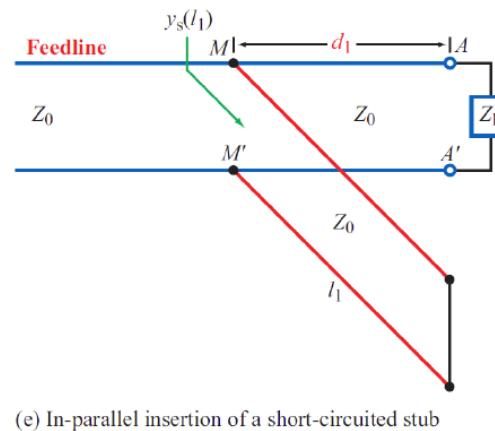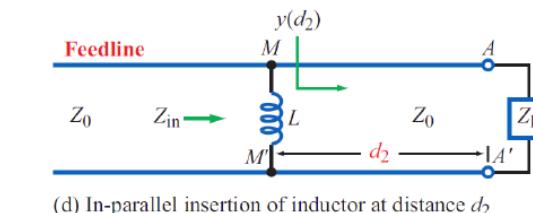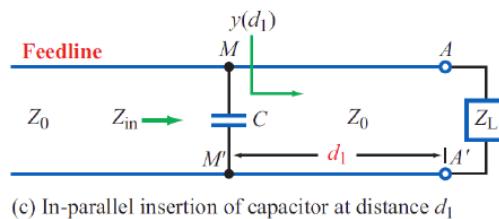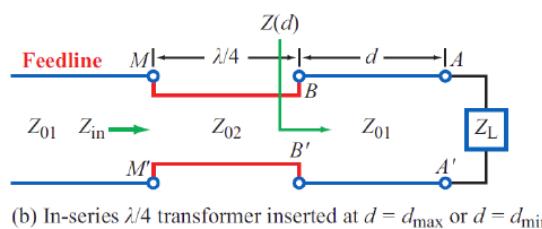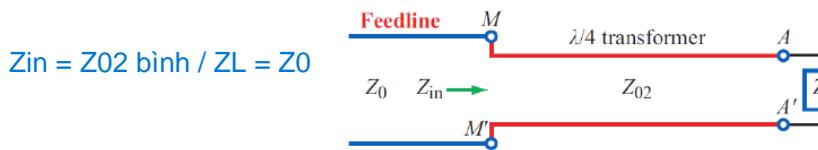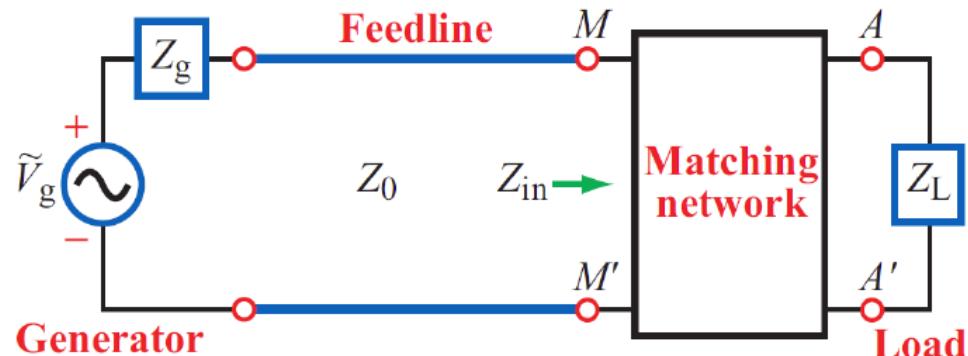
# 4. Impedance Matching

- The purpose of the matching network is to eliminate reflections at terminal MM' for wave incident from the source. Even though multiple reflections may occur between AA' and MM', only a forward travelling wave exists on the feedline.




# 4. Impedance Matching
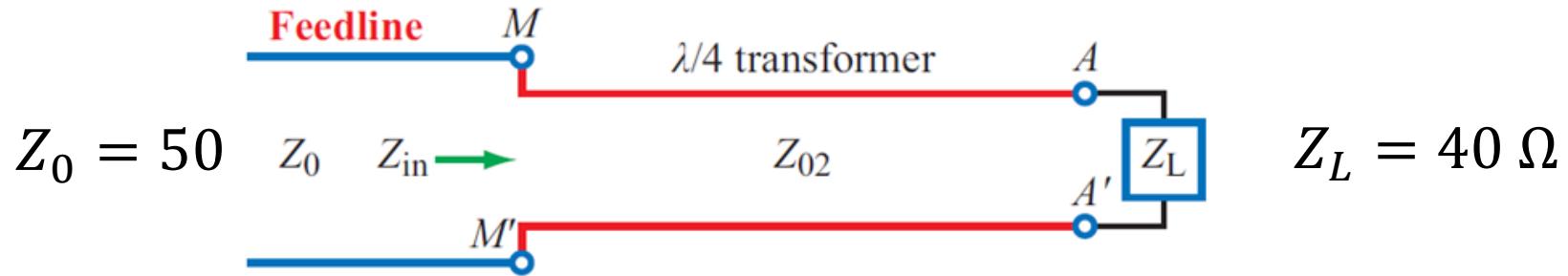
## A. Quarter wavelength Transformer Matching:




❖ In case of complex impedance:

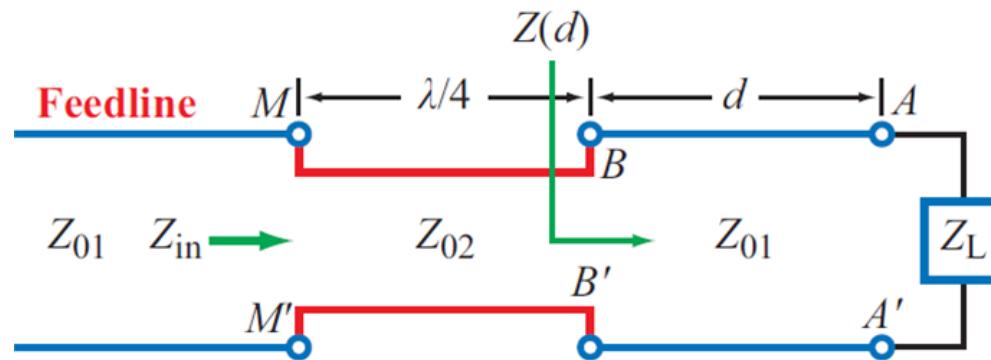


# 4. Impedance Matching

## Example:

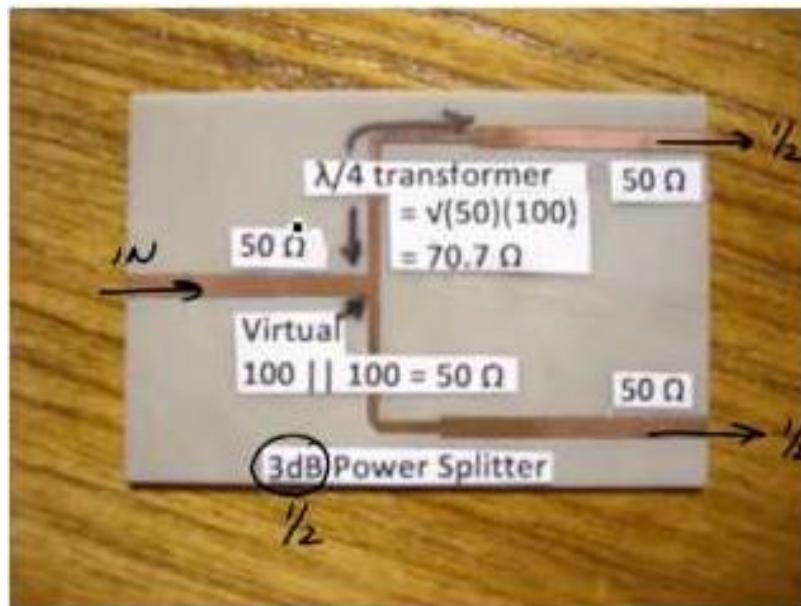


- ❖ A simple but accurate equation for Microstrip Characteristic Impedance:
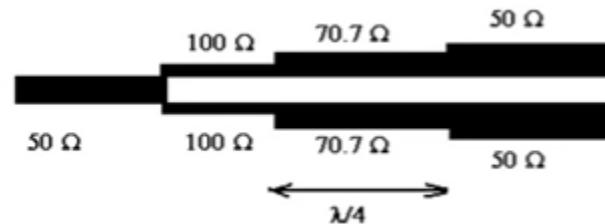
$$Z_0 = \frac{60}{\sqrt{\epsilon}} \ln \left( \frac{8h}{W} + \frac{W}{4h} \right) \quad \text{for } W \leq h$$



# 4. Impedance Matching

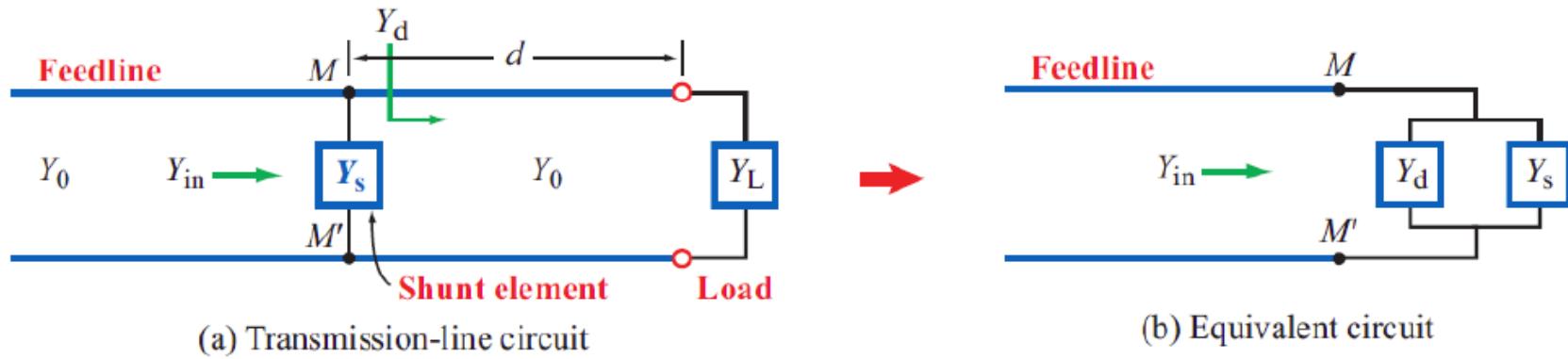**B. Lumped-Element Matching:** choose  $d$  and  $Y_s$  to achieve a match at  $MM'$ .



❖ The input admittance at  $MM'$  can be written as:

$$Y_{in} = Y_d + Y_s = (G_d + jB_d) + jB_s$$

❖ To achieve a matched condition at  $MM'$ , it is necessary that  $y_{in} = 1$ , which translates into two specific conditions, namely:


$$g_d = 1$$

$$b_s = -b_d$$

# 4. Impedance Matching



**B. Lumped-Element Matching:** choose  $d$  and  $Y_s$  to achieve a match at  $MM'$ .

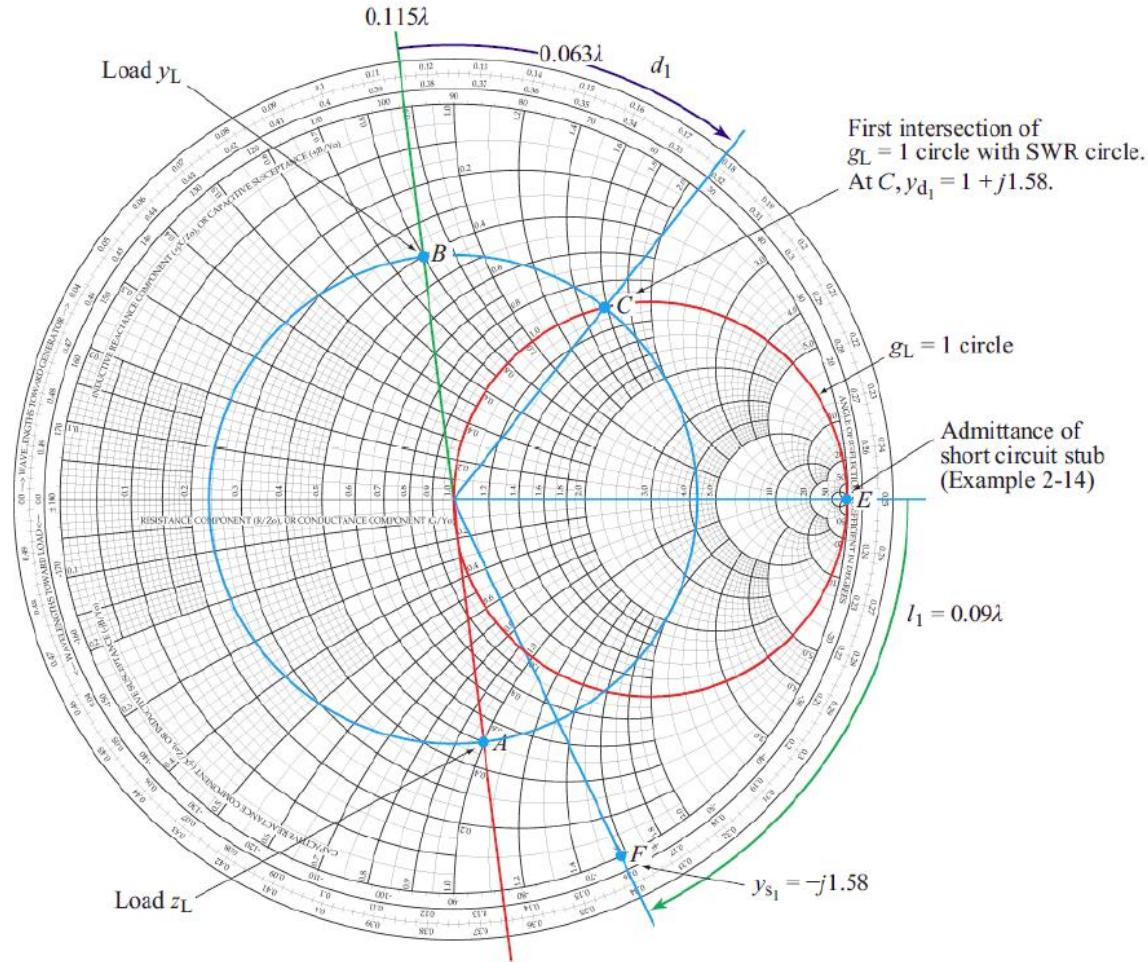Example 9: A load impedance  $Z_L = 25 - j50\Omega$  is connected to a  $50\Omega$  T.L. Insert a shunt element to eliminate reflections towards the sending end of the line. Specify the insert location  $d$  (in wavelengths), the type of element and its value, given that  $f = 100MHz$ .




# 4. Impedance Matching

C. Single Stub Matching: choose  $d$  and length of stub  $l$  to achieve a match at  $MM'$ .

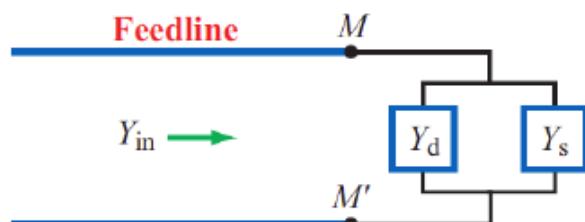
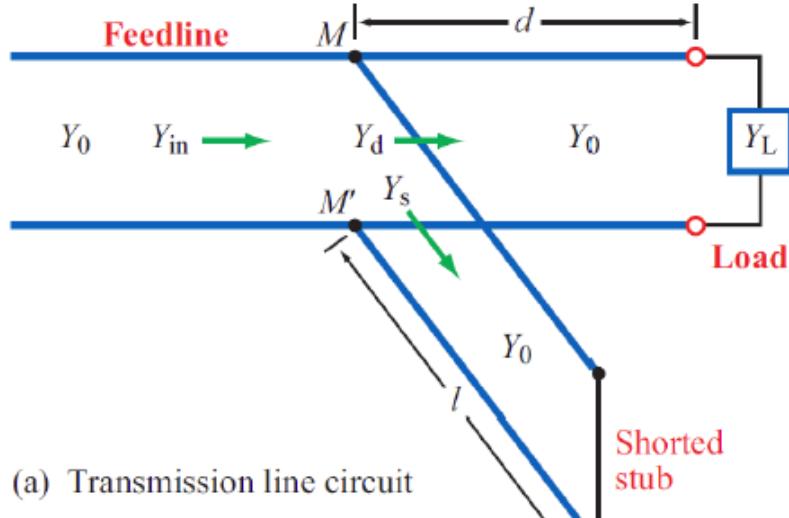


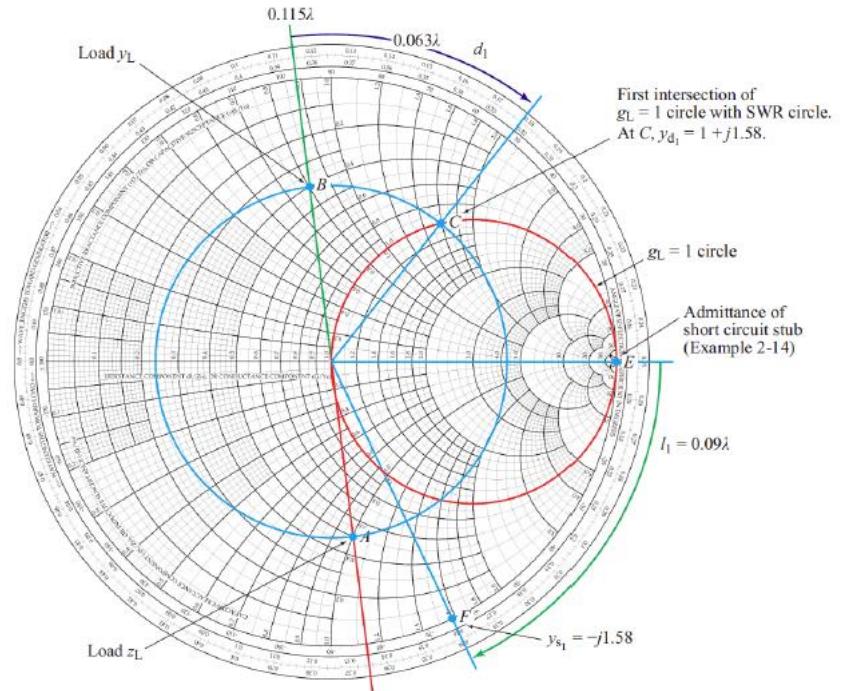Example 10: Repeat Example 9 but use a shorted stub to match the load impedance.




# More Examples

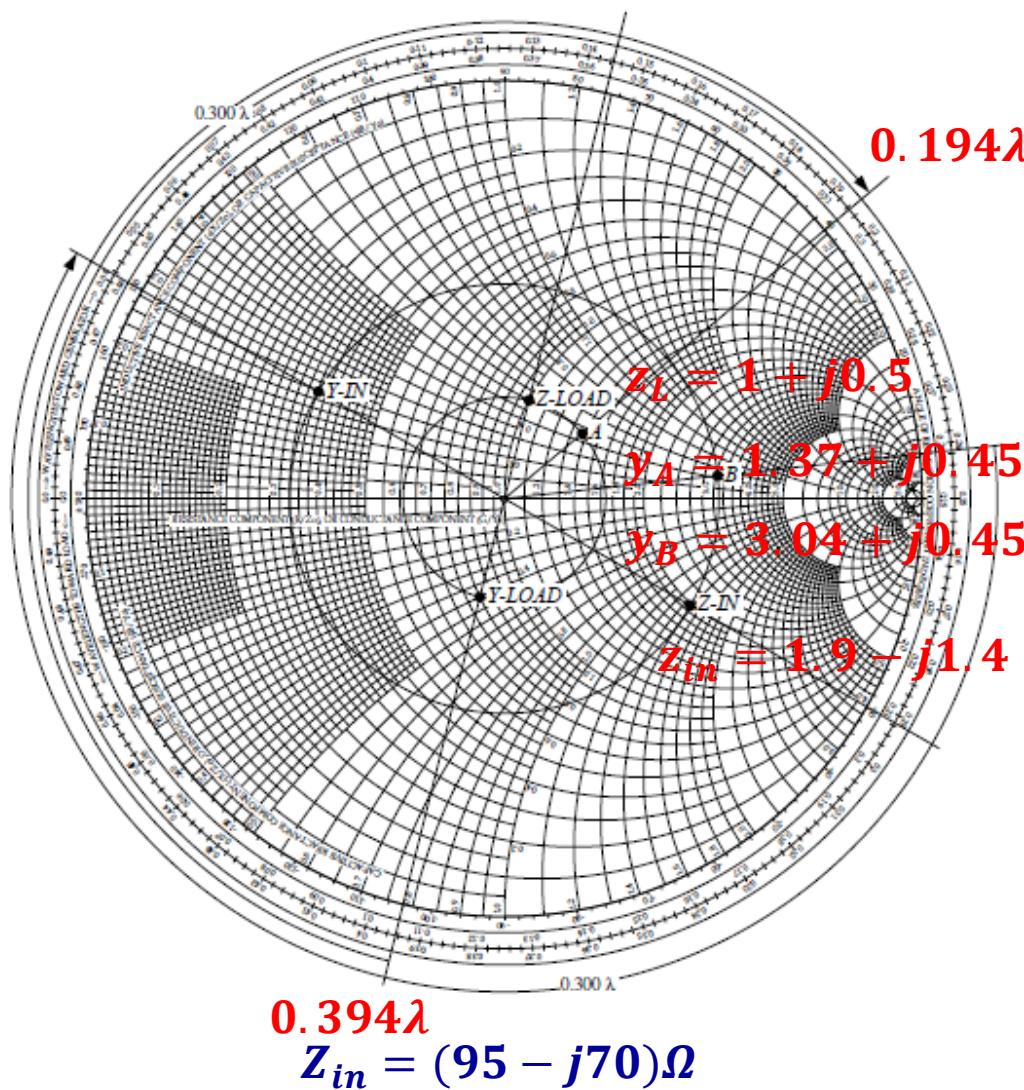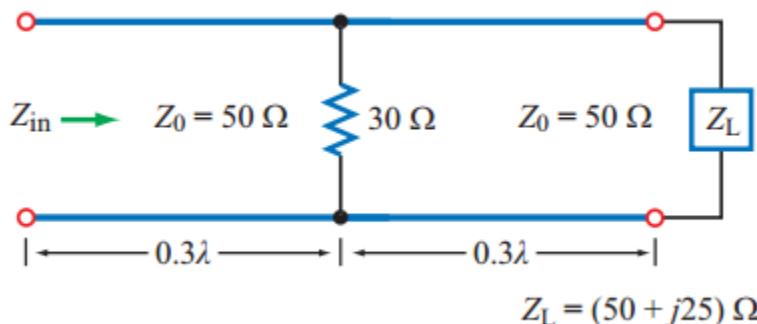**Example 11:** A  $50\Omega$  lossless line  $0.6\lambda$  long is terminated in a load with  $Z_L = (50 + j25)\Omega$ . At  $0.3\lambda$  from load, a resistor with resistance  $R = 30\Omega$  is connected as shown in following figure. Use the Smith Chart to find  $Z_{in}$ .




# More Examples

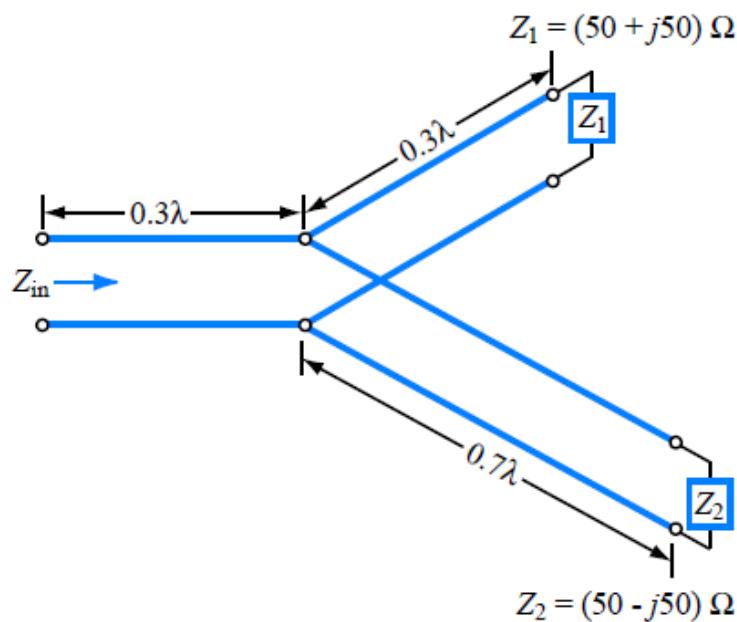**Example 12:** Use the Smith Chart to find  $Z_{in}$  of the  $50\Omega$  feedline shown in following figure.



$$Z_{in} = (82.5 - j89.5)\Omega$$

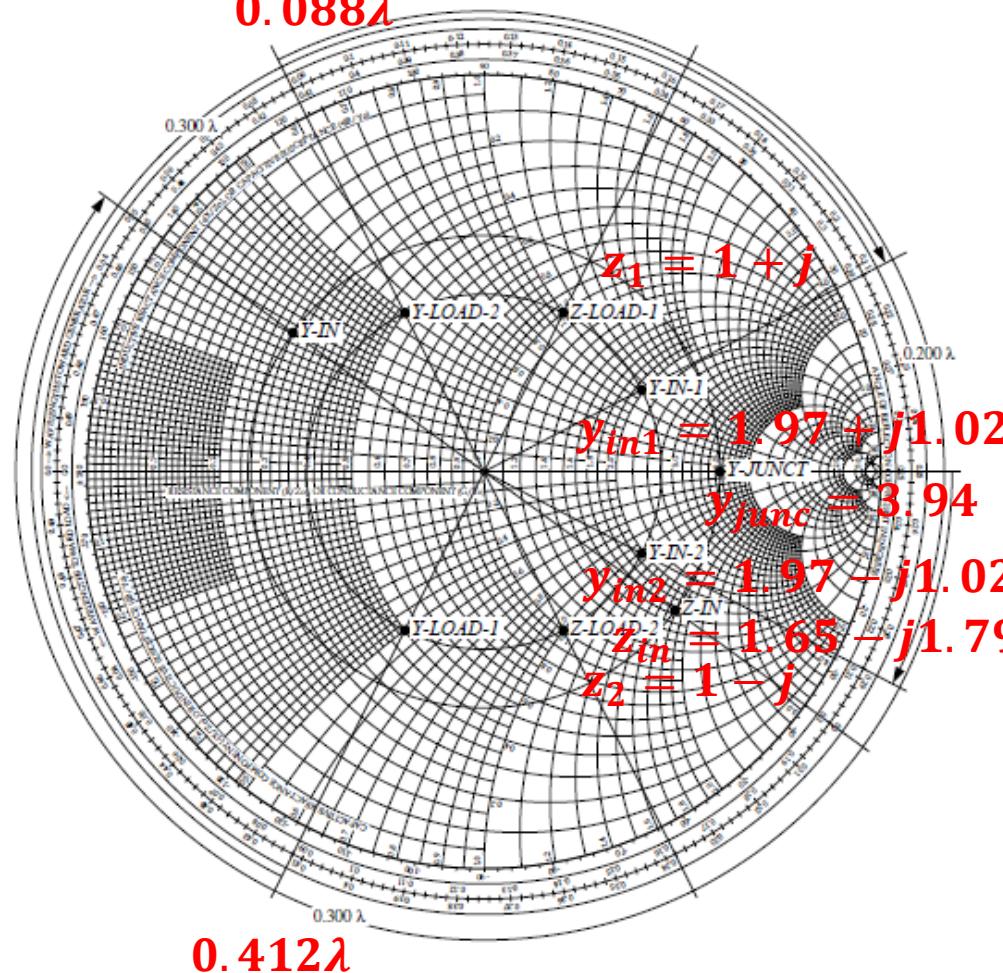


# More Examples

**Example 13:** A  $50\Omega$  lossless line is to be matched to an antenna with  $Z_L = (75 - j20)\Omega$  using a shorted stub. Use the Smith Chart to determine the stub length and distance between the antenna and stub.

$$0.077\lambda$$

$$0.041\lambda$$

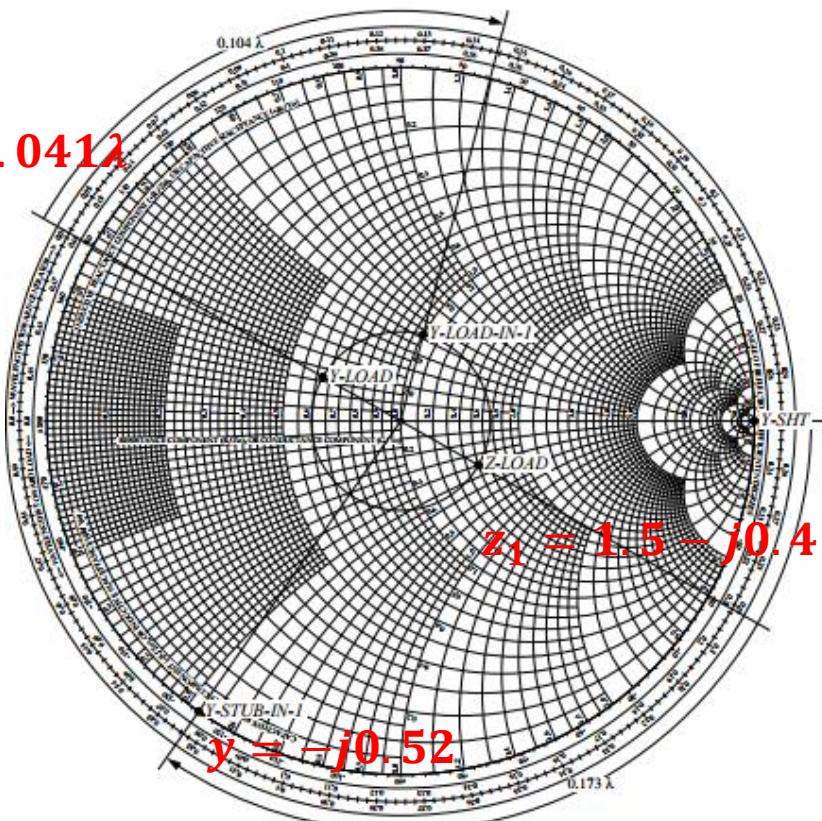

$$Z_1 = 1.5 - j0.4$$


$$\gamma = -j0.52$$

$$d_1 = 0.104\lambda, l_1 = 0.173\lambda$$

$$Z_1 = 1.5 - j0.4$$

$$0.327\lambda$$
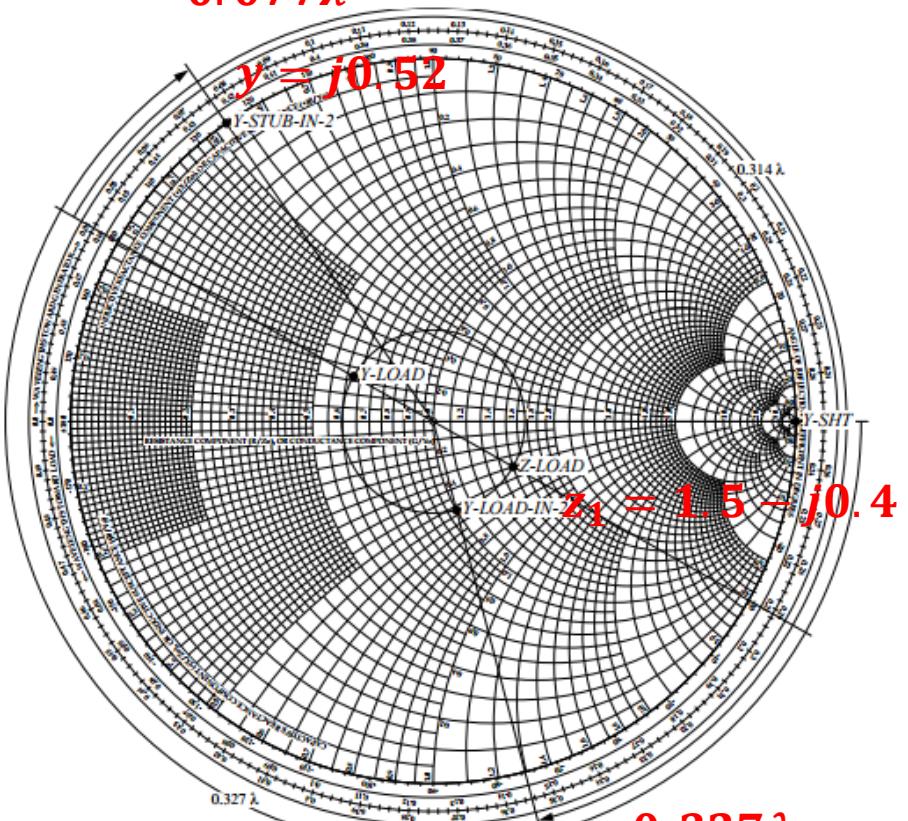
$$d_2 = 0.314\lambda, l_2 = 0.327\lambda$$



$$\gamma = j0.52$$

# Q&A